

# Electric Circuit & Systems

classmate

Date \_\_\_\_\_  
Page \_\_\_\_\_


→ Network

No close path for flow of current.


→ Circuit

Closed path for flow of current. (sp. kind of network)  
(atleast 1)

⇒ Every circuit is a network.

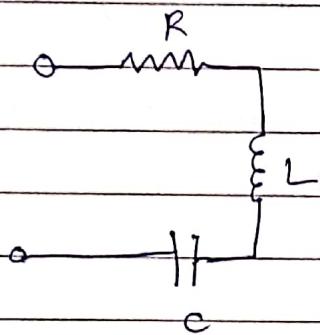

Network

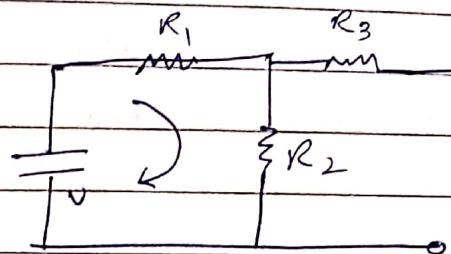

Circuit

⇒ System

different

→ Combination of network & circuit who work together to fulfil a objective.

Units :

Unit 1 - Electric circuit

(consists of one or more elements)

DC & AC circuit.

DC → <sup>↑</sup> Source .

AC → source .

Analysis

I/p Jouny o/p


input known  
& circuit parameters

Synthesis

I/p circuit o/p

determine circuit  
parameters

Eg: Conversion of 200V to 100V.

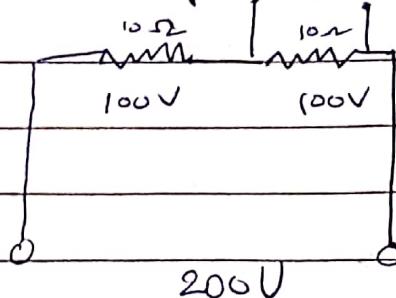

- Charge do not take place for long time, then it is static state
- Charge takes ~~for~~ place in circuit after working, then it is transient state.

⇒ DC & AC circuit analysis

Resistance: Obs. to flow of current.

Inductance: Obstruction to change of current.

Capacitance: opposes the change of voltage.

↑ ↓ never connect in d.c. circuit.

AC (all elements)

⇒ Unit 2 → Magnetic circuit

⇒ Unit 3 → electrical machines (m/c).

Machines - saves human effort. (any equipment)

↓ For

Electrical energy  $\rightarrow$  mech. energy

Electrical machines is a device which

→ If electrical energy  $\rightarrow$  mech. energy.  
motor

generator.

## ⇒ Unit 4 - Semiconductor devices

diode, transistor

silicon controlled rectifiers.

MOSFET

half wave ] rectifier  
full wave

## ⇒ Unit 5 - Digital electronics

Logic gates

flip flops → memory card is made up  
of flip flops

Adder

Subtractor

# Unit 1

## Electrical Circuits

$\text{EMF} \rightarrow \text{minimum P.D}$

$V \rightarrow \text{P.D}$

Ohm's law

$$V \propto I$$

$$V = RI$$

- every voltage cannot be emf.
- emf always across generating source.
- Voltage is potential diff. due to which current flows.  
↳ rate of flow of charge.

→ Electric elements:-

### Active

→ gives energy  
to circuit  
(sources).

↳ give energy  
to system.  
(energy law)

one energy → elec. energy  
(elec. source)

### Passive

→ which consumes  
labour energy  
& store it.

- Resistance
- Inductance
- Capacitance


\*⇒ Classification of Sources:

### Independent

are those whose  
output not affected  
by change in  
circuit parameter
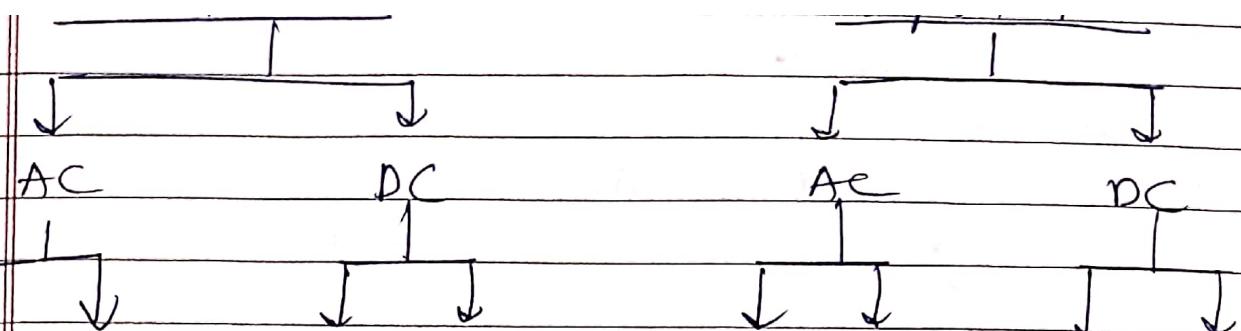
### dependent

output is  
affected by  
change in circuit  
parameters.



Voltage source      Current source      VS      CS

VS      CS      VS      CS


(provides sp. source

constant which delivers

voltage current in circuit)


to the circuit).

$\Rightarrow$  Independent Sources:

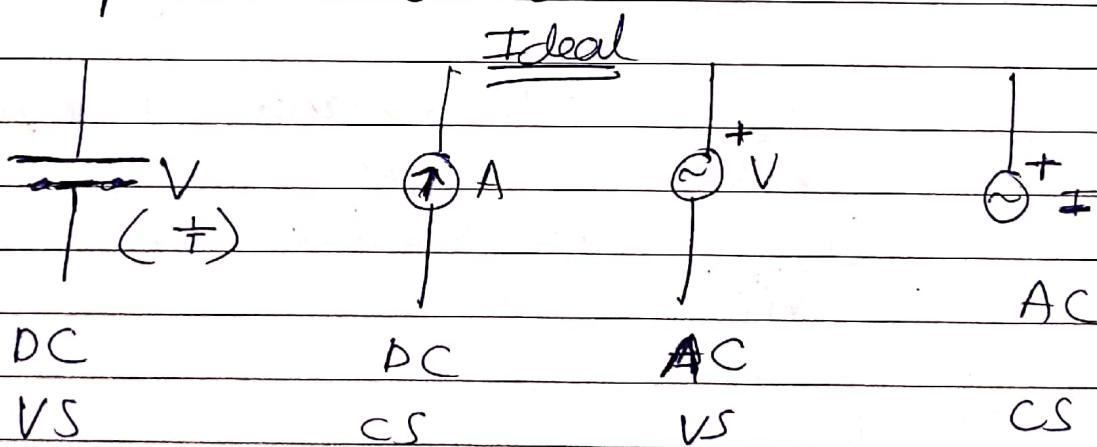

$\Rightarrow \phi \rightarrow$  phase

Sources

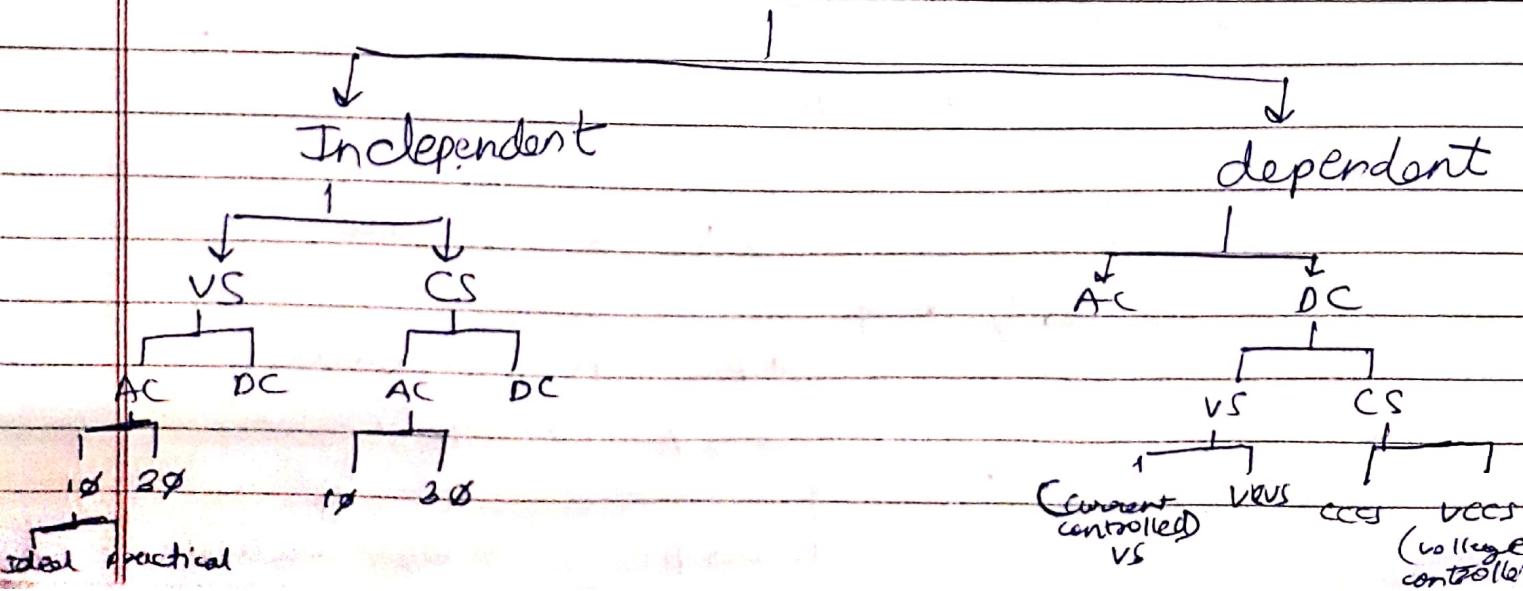

$\Rightarrow$  Internal Resistance



d.c. source  $\rightarrow 0$

Ideal  $\rightarrow 0$

Ideal  $\dagger$

Internal Impedance (AC)


dc.  $\rightarrow 0$ .

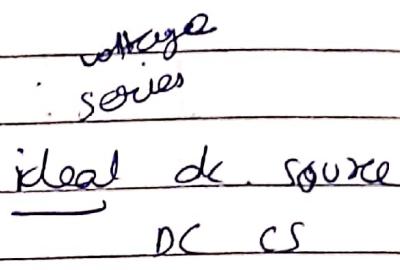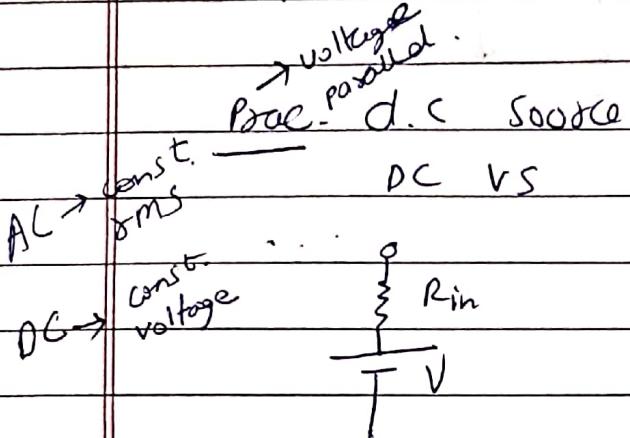


$\Rightarrow$  Source: any equipment that converts non-electrical energy to electrical energy.

$\Rightarrow$  Ideal  $\dagger$  Source: int. resistance or impedance  $(VS)(AC)$  is zero.

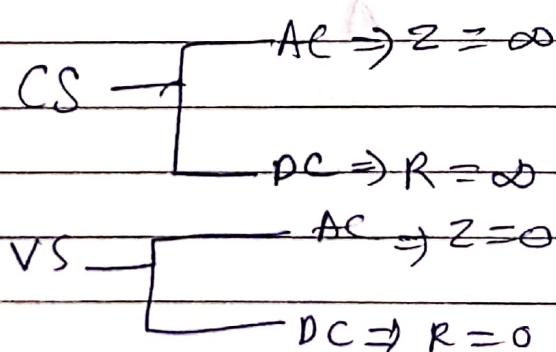Source: int. resistance or impedance  $(VS)(DC)$  is  $\infty$ .




Practical

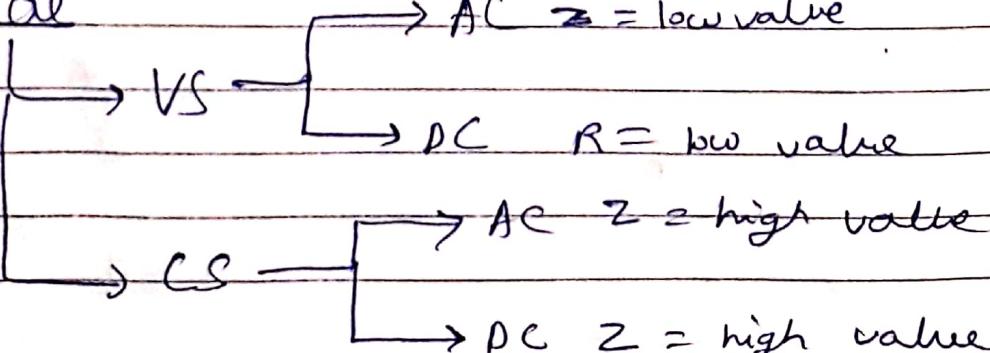


⇒ Dependent Sources:


CCVS

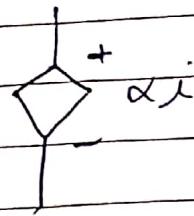


CCCS

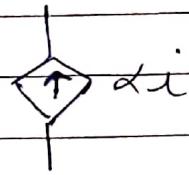

VCVS

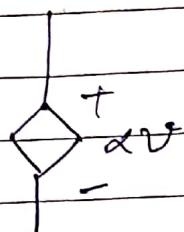


VCCS

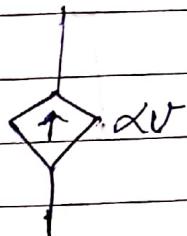

Symbols:

independent source:

DC source (VS)

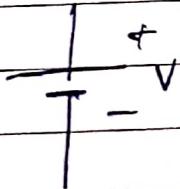

DC current



ideal


ideal sources

$\left\{ \begin{array}{l} R_{in} \\ T \end{array} \right.$

$V$  -  $B_{ac}$ .

practical source.


Ideal sources

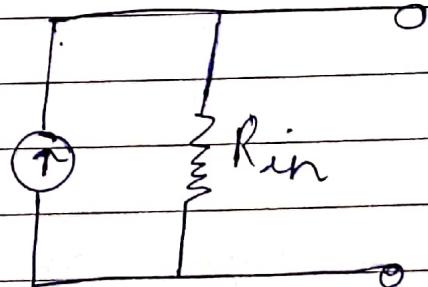


practical

⇒ AC source (Independent):

VS

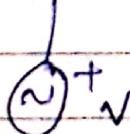

ideal

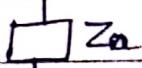


Practical

CS




Ideal

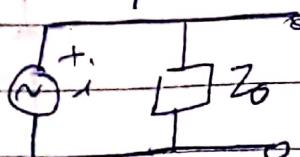


Practical

⇒ Characteristics of sources:


Ideal (Vs)

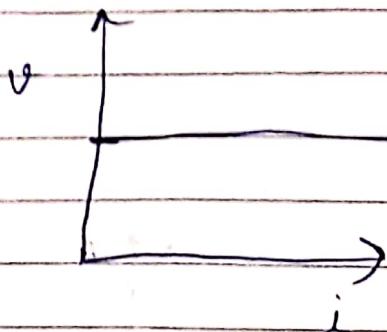


Practical (Vs)

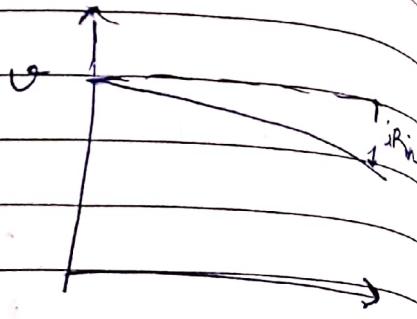

Ideal (Cs)

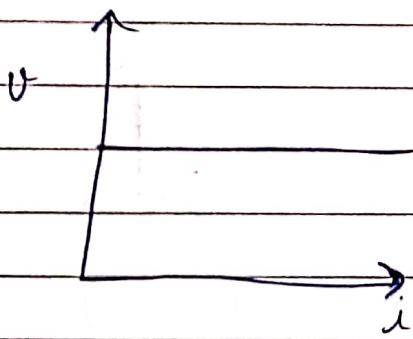

Practical (Cs)

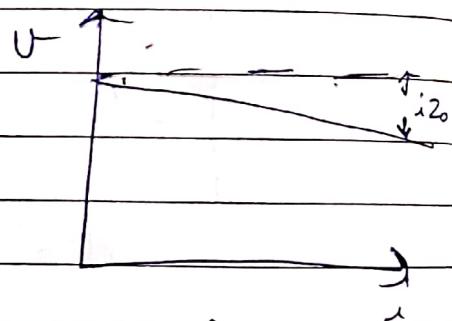


Open (Z<sub>o</sub>)


⇒ Types of Connections:

- 1) Series → current remains same, voltage divides. (Resist.)
- 2) Parallel → current divides, voltage same (Resist. ↓)
- New 3) Star Delta

Ans

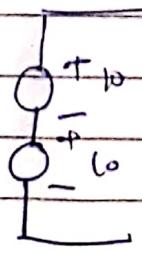


$$V = V_1 + V_2 = 20V$$

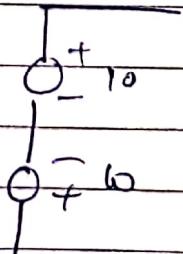


$$V = 0V,$$



$\Rightarrow$  Star Delta Connection:

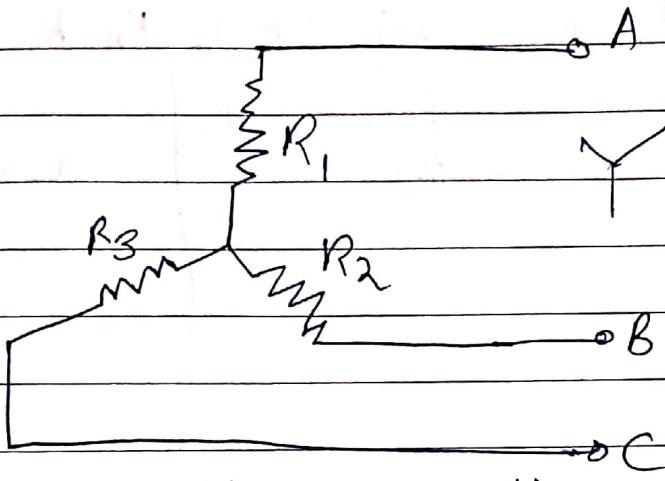

Star connection

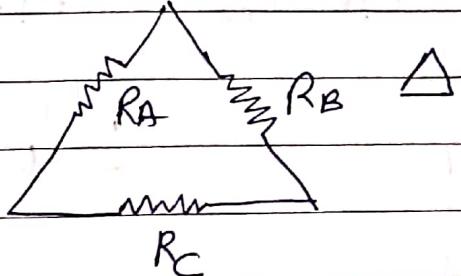

Delta connection

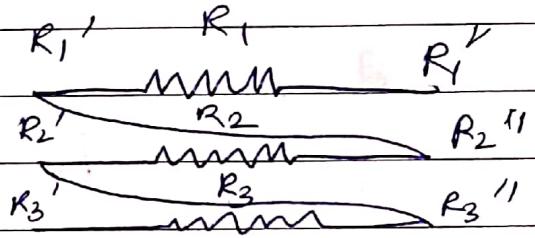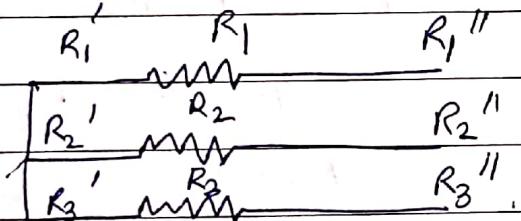

Delta connection

Delta - Star

$\Rightarrow$  Star-Delta Conversion:

$$R_{ABY} = R_1 + R_2$$

$$R_{BCY} = R_2 + R_3$$

$$R_{ACY} = R_1 + R_3$$



$$R_{ABA} = \frac{R_2(R_1 + R_3)}{R_1 + R_2 + R_3}$$

$$R_{BCA} = \frac{R_3(R_1 + R_2)}{R_1 + R_2 + R_3}$$

$$R_{BCD} = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$

$$R_{ACD} = \frac{R_1(R_2 + R_3)}{R_1 + R_2 + R_3}$$



$$R_{ABY} = R_{ABD}$$

$$R_{ACY} = R_{BCD}$$

$$R_{ACY} = R_{ACD}$$

$$R_A + R_B = \frac{R_1 R_2 + R_2 R_3}{R_1 + R_2 + R_3}$$

(1)

$$R_B + R_C = \frac{R_1 R_3 + R_2 R_3}{R_1 + R_2 + R_3}$$

(2)

$$R_A + R_C = \frac{R_1 R_2 + R_1 R_3}{R_1 + R_2 + R_3}$$

(3)

Add (1) & (3) - (2)



$$R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

Add (1) & (2) - (3)

$$R_C = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

Add (1) & (2) - (1)

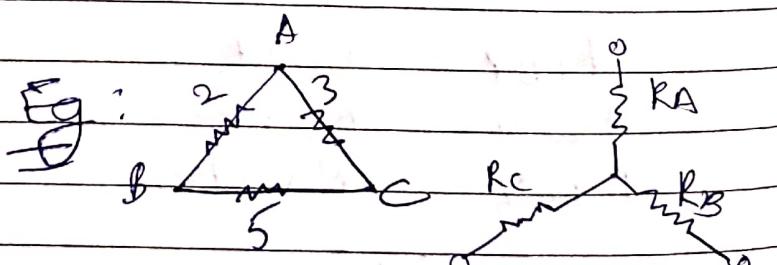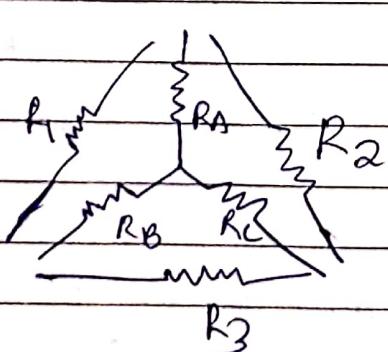

$$RA = \frac{2 \times 3}{2 + 3 + 5} = \frac{6}{10} = 0.6 \Omega$$

$$RB = 1.5 \Omega$$

$$RC = 1 \Omega$$

$\Rightarrow$  Star to Delta Conversion:

$$R_A = \frac{R_1 R_2}{R_1 + R_2 + R_3} \quad \text{--- (4)}$$

$$R_B = \frac{R_2 R_3}{R_1 + R_2 + R_3} \quad \text{--- (5)}$$

$$R_C = \frac{R_1 R_3}{R_1 + R_2 + R_3} \quad \text{--- (6)}$$

$$R_A R_B + R_B R_C + R_C R_A$$

$$= \frac{R_1 R_2^2 R_3}{(R_1 + R_2 + R_3)^2} + \frac{R_2 R_1 R_3^2}{(R_1 + R_2 + R_3)^2} + \frac{R_1^2 R_2 R_3}{(R_1 + R_2 + R_3)^2}$$

$$= \frac{R_1 R_2 R_3 (R_1 + R_2 + R_3)}{(R_1 + R_2 + R_3)^2}$$

$$= \frac{(R_1 + R_2) R_3}{R_1 + R_2 + R_3} \rightarrow R_A$$

$$\frac{R_A R_B + R_B R_C + R_C R_A}{R_A} = R_3$$

$$\therefore R_3 = R_B + \frac{R_B R_C}{R_A} + R_C$$

$$R_1 = R_A + R_C + \frac{R_A R_C}{R_B}$$

$$\therefore R_2 = \frac{R_A R_B}{R_C} + R_B + R_A$$

$$R_1 = 10 + 2.5 = 12.5 \Omega$$


$$R_2 = 15 + 10 = 25 \Omega$$

$$R_3 = 15 + 10 = 25 \Omega$$

$\Rightarrow$  Current & Voltage division rule:

$\rightarrow$  Voltage division: Works only in series  
rule

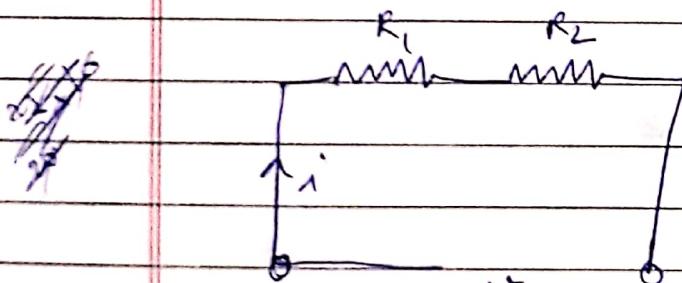Voltage divides in elements of series connection



$$R = R_1 + R_2$$

$$i = \frac{V}{R}$$

$$R_1 + R_2$$

$$\rightarrow V_{R_1} = i R_1$$

$$= \frac{V}{R_1 + R_2} \cdot R_1$$

$$R_1 + R_2$$


$$\rightarrow V_{R_2} = i R_2$$

$$= \frac{V}{R_1 + R_2} \cdot R_2$$

$$R_1 + R_2$$

$\rightarrow$  Current division formula/Rule:

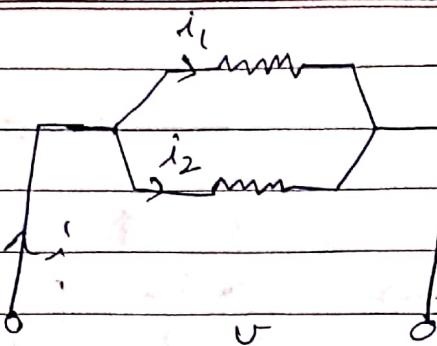Useful to determine current in elements connected in parallel.




$$\rightarrow R = \frac{R_1 R_2}{R_1 + R_2}$$

$$\rightarrow i = \frac{V(R_1 + R_2)}{R_1 R_2} \Rightarrow i = \frac{V}{R_1 + R_2}$$

$$\therefore i_1 = \frac{V}{R_1}, \quad i_2 = \frac{V}{R_2}$$

$$\therefore i_1 = \frac{VR_2}{R_1 + R_2}, \quad i_2 = \frac{VR_1}{R_1 + R_2}$$

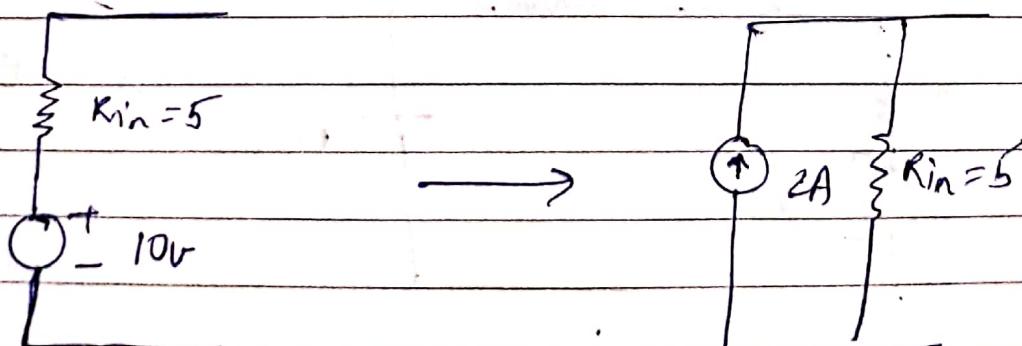$\Rightarrow$  Source transformation: Transformation of Source




V.S

$$i = 2A$$


C.S.

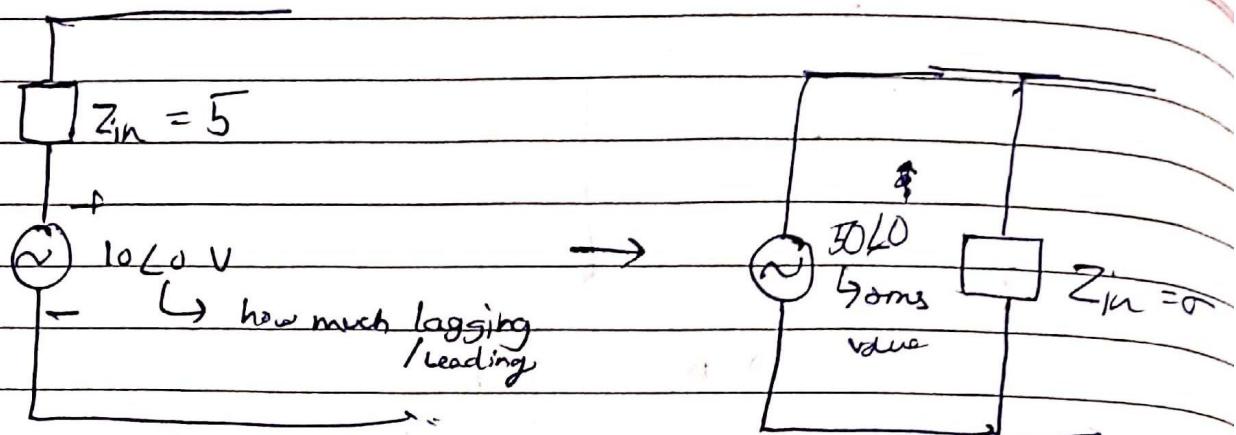N.S  $\rightarrow$  C.S possible when  $R_{in}$  connected in series.




VS

CS.

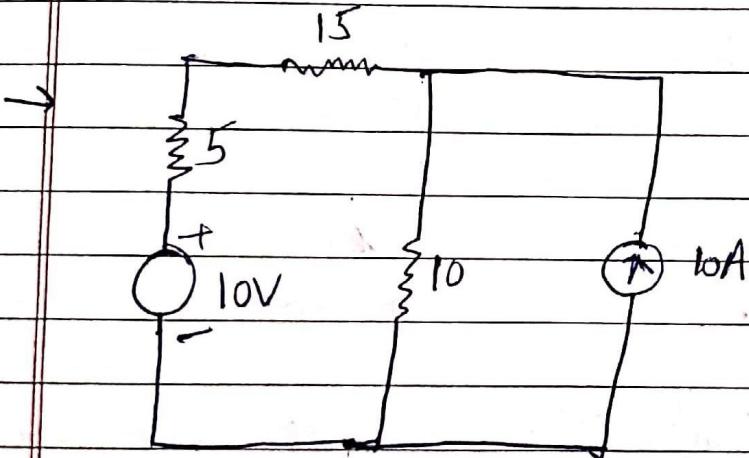


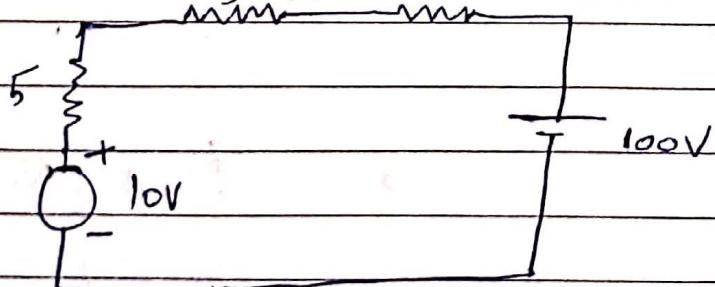by applying CS to VS transformation method



$$i = \frac{10 - 100}{30} A.$$

Q-

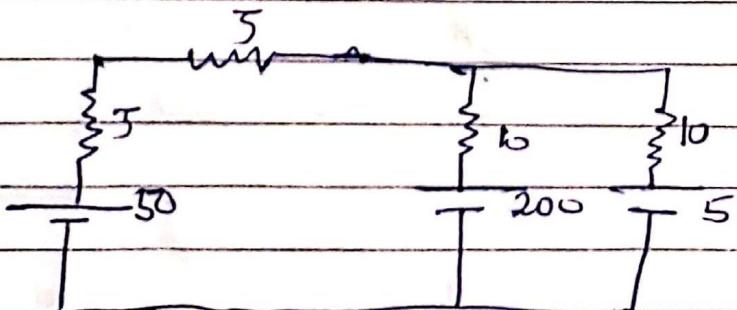

⇒ Kirchoff's law:

1) Kirchoff's current law:

Junction Rule / Conservation of charge.


2) Kirchoff's voltage law:

/ Voltage law

→ Junction at which two or more elements are connected is node.

→ Link b/w <sup>two</sup> nodes is called Branch.

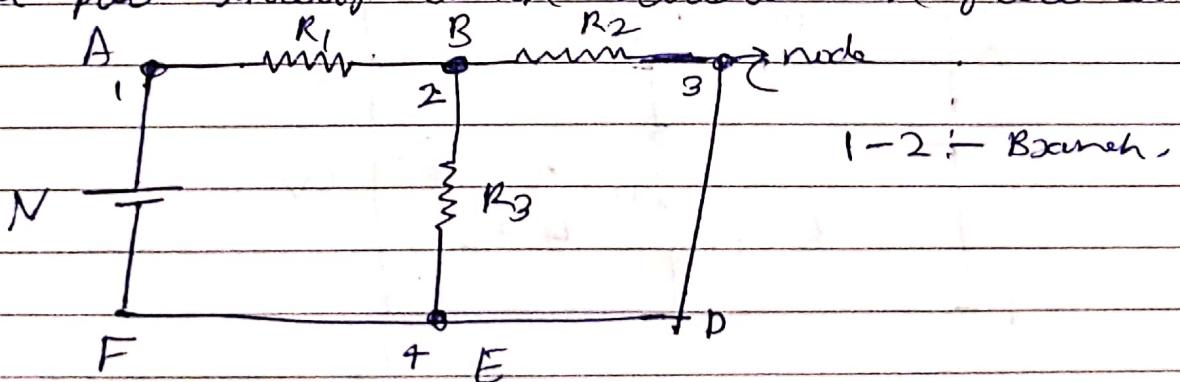
→ Closed path through which current can flow is loop



⇒ Special kind of loop which doesn't have any other closed <sup>subset</sup> inside it is called Mesh.

⇒ Every mesh is a loop, but every loop is not a mesh.

⇒ Mesh Analysis / Maxwell loop method:

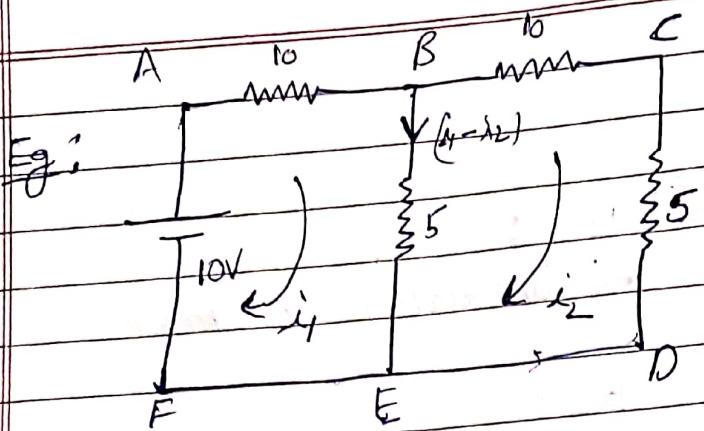


mesh 1 ABEFA

mesh 2 BCDEB

$$-10i_1 - 5(i_1 - i_2) + 10 = 0 \quad \text{---(1)}$$
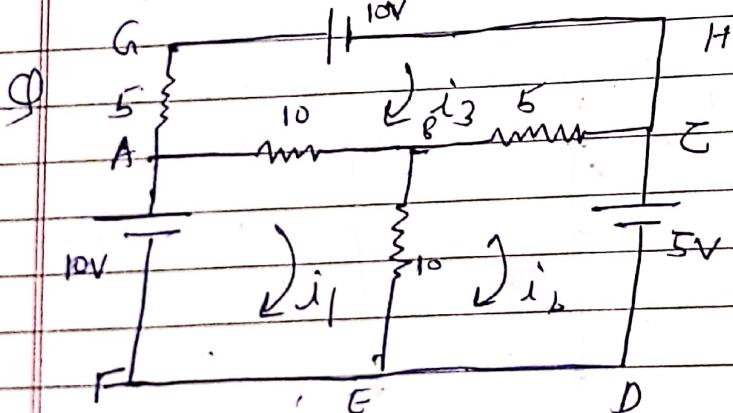
$$+ 5(i_1 - i_2) + 5i_2 - 10i_2 = 0 \quad \text{---(2)}$$



mesh 1 ABEFA

$$10 - 10(i_1 - i_3) - 10(i_1 - i_2) = 0.$$


Mesh 2 BCDEB

$$-5 - 5(i_2 - i_3) - 10(i_2 - i_1) = 0$$

Mesh 3 GHKBAG

$$-10 - 5(i_3 - i_1) - 10(i_3 - i_1) - 5i_3 = 0 \Rightarrow$$

## → Super Mesh Analysis:

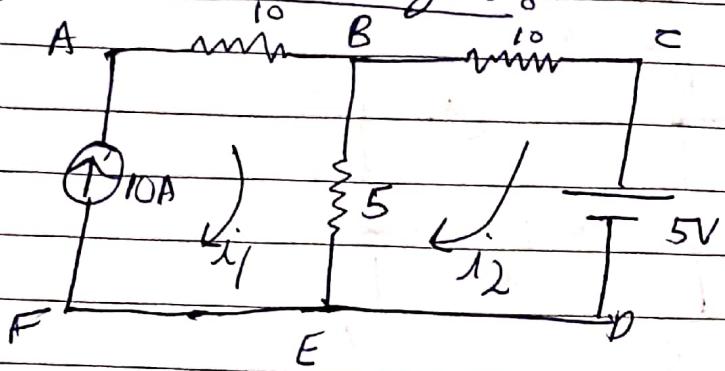


Mesh 2 BCDEB

$$-5 - 5(i_2 - i_1) - 10i_2 = 0$$

Mesh ABEFA

$$i_1 = 10A$$

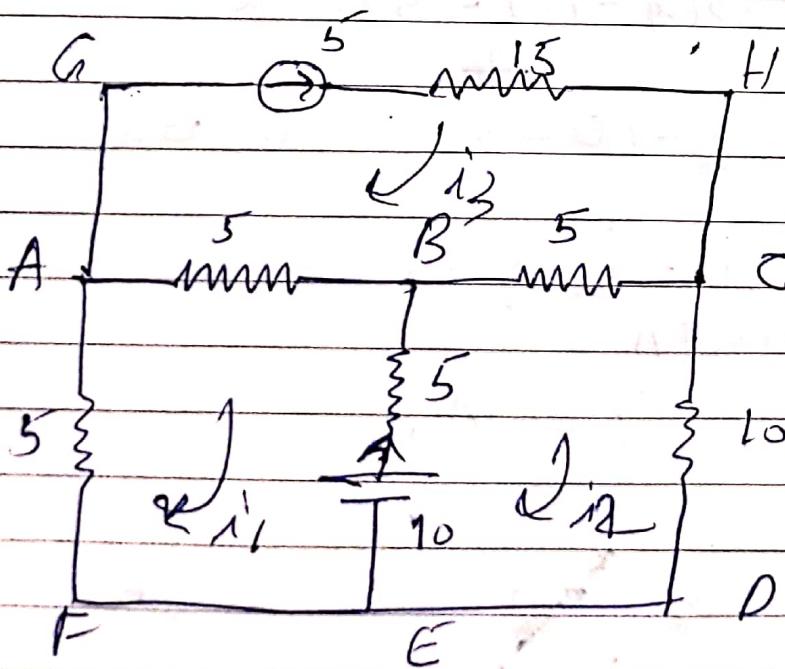↳ C.S. (every branch has the same current)



→ Mesh 3 GHESAG


$$i_3 = 5.$$

→ Mesh 1 ABEFA

$$-5i_1 - 5(i_1 - i_3) - 5(i_1 - i_2) - 10 = 0$$

→ Mesh 2 BCDEB
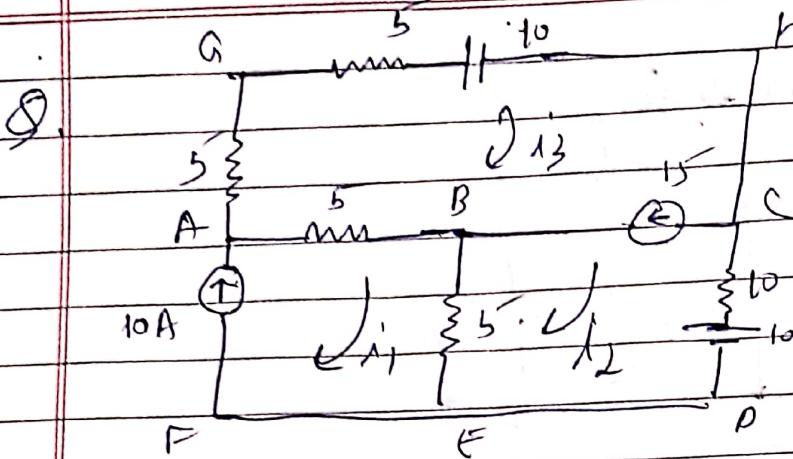
$$10 - 5(i_2 - i_1) - 5(i_2 - i_3) - 10i_2 = 0$$



→ Super mesh is combination of two or more than two meshes having current source common

Super mesh ~~BED~~ BE'DCHGAB

$$-5(i_1 - i_2) - 5i_2 - 10$$


+

$$-5i_2 - 10 - 5(i_3 - i_1) = 0,$$

$$i_3 - i_2 = 15$$

mesh ABFEA

$$i_1 = 10A.$$

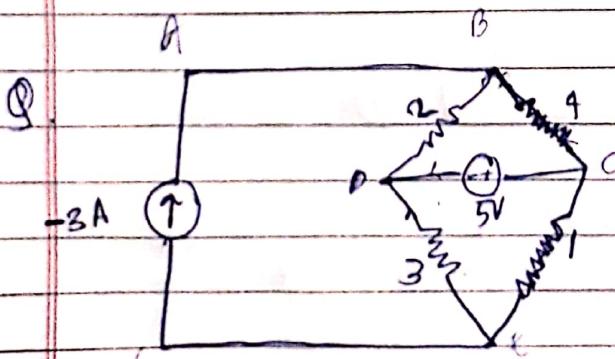

Mesh ABC.EFA


$$i_1 = -3,$$

$$-2(i_1 - i_2) - 4i_2$$

$$+ -3(i_3 - i_1) - i_3 = 0$$

$$i_3 - i_2 = 5$$

## Nodal Analysis:

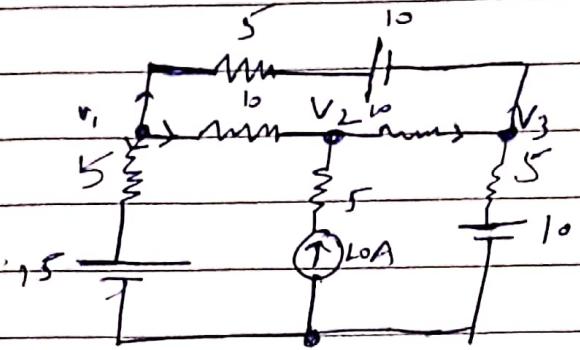

KCL at node 1:


$$\frac{V_1 - 15}{5} + \frac{V_1 - V_2}{10} + \frac{V_1 - 10 - V_3}{5} = 0 \quad \text{--- (1)}$$

KCL at node 2:

$$\frac{V_2 - V_1}{10} + \frac{V_2 - V_3}{10} - \frac{10}{10} = 0 \quad \text{--- (2)}$$

KCL at node 3:
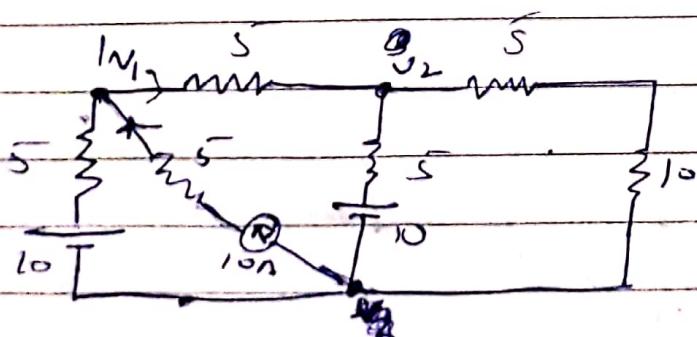
$$\frac{V_3 - V_2}{10} + \frac{V_3 - 10}{5} + \frac{V_3 + 10 - V_1}{5} = 0. \quad \text{--- (3)}$$




KCL at node 1:

$$\frac{V_1 - 10}{5} + \frac{V_1 - V_2}{5} - \frac{10}{10} = 0$$

KCL at node 2:
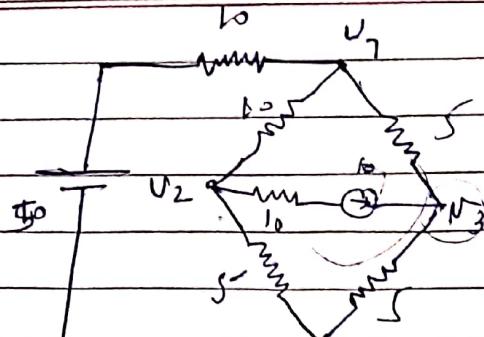
$$\frac{V_2 - V_1}{5} + \frac{V_2 - 10}{10} + \frac{V_2 - 0}{10} = 0$$



KCL at node 1:

$$\frac{V_1 - 5}{10} + \frac{V_1 - V_2}{10} + \frac{V_1 - V_3}{5} = 0 \quad \textcircled{1}$$


KCL at node 2:

$$\frac{V_2 - 10}{10} + \frac{V_2 - 0}{10} + \cancel{\frac{V_2 - V_3}{5}} + 10 = 0 \quad \textcircled{2}$$

+ KCL at node 3:

$$\frac{V_3 - V_1}{5} + \frac{V_3 - 0}{10} + 10 = 0 \quad \textcircled{3}$$

node 2 & node 3 make supernode.

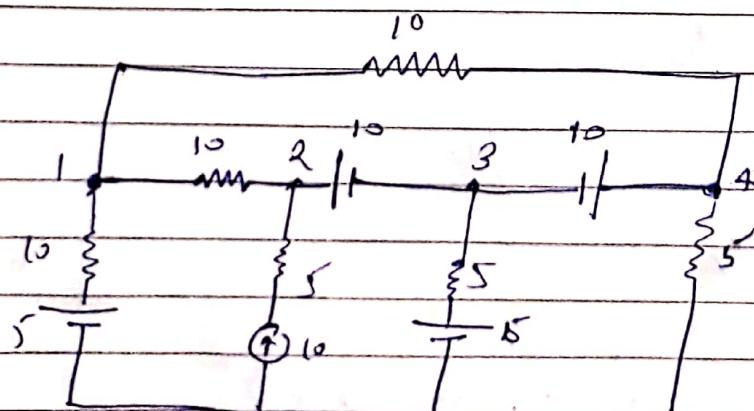

Supernode at 2, 3, 4

$$\frac{V_2 - V_1}{10} + \frac{V_3 - 15}{5} + \frac{V_4 - V_1}{10} + \frac{V_4 - 0}{5} = 0 \quad \textcircled{1}$$

$$V_2 - V_3 = 10 \rightarrow \textcircled{2}$$

$$V_4 - V_3 = 10 \rightarrow \textcircled{3}$$


KCL for node 1:


$$\frac{V_2 - V_1}{10} + \frac{V_1 - 5}{10} + \frac{V_1 - V_4}{10} = 0 \rightarrow \textcircled{4}$$

$\Rightarrow$  Thevenin's Theorem:

$\rightarrow$  Types of network:

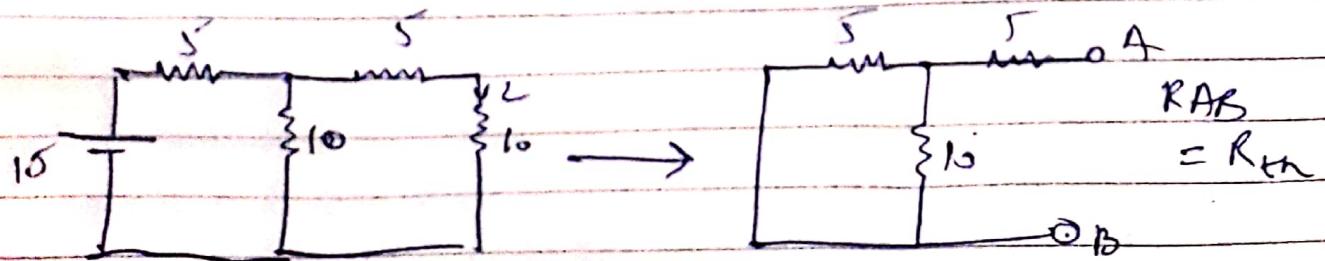- 1) Active & passive network.
  - 2) Linear & non-linear network.  
 ↳ input & output      ↳ output  $\propto \frac{1}{\text{input}}$ .  
 (not directly).
  - 3) Lumped & distributed network.
  - 4) unilateral & bilateral  
 ↳ work in one dir.      ↳ work in both dir.
- Any active linear bilateral network can be replaced by Thevenin's equivalent circuit having a net series combination of Thevenin voltage  $V_{th}$  & Thevenin resistance of  $R_{th}$ .




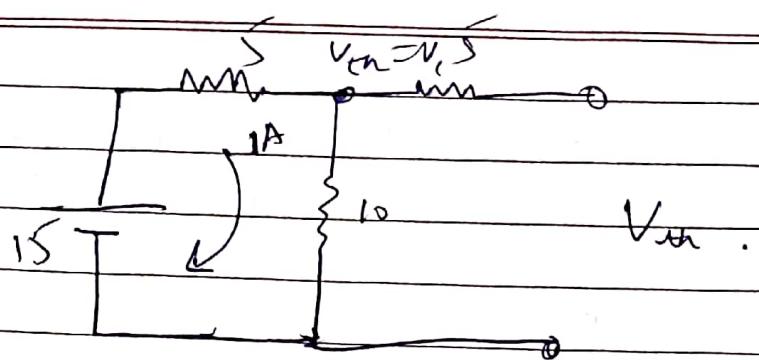


$$V_{10} = 10 + 1 \times 10V$$


$$V_{10} = 10V$$

$$\frac{V_1 - 15}{5} + \frac{V_1 - 0}{10} = 0$$

$$V_1 = V_1 = V_{10}$$

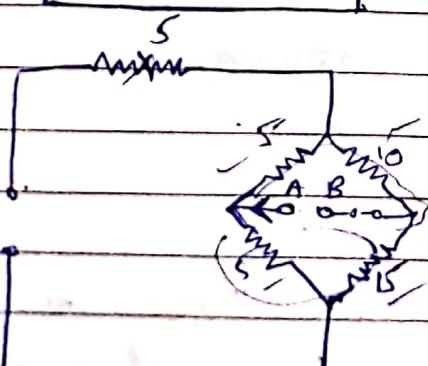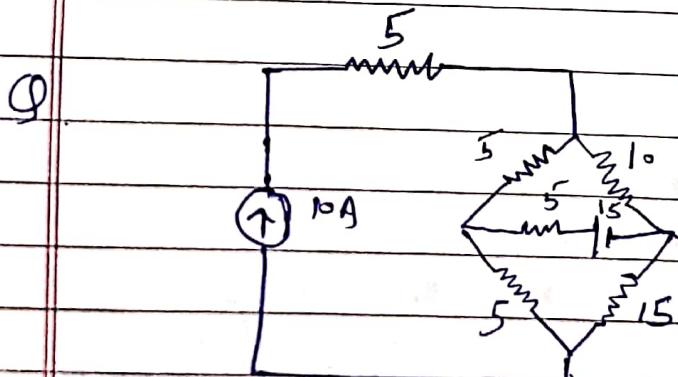
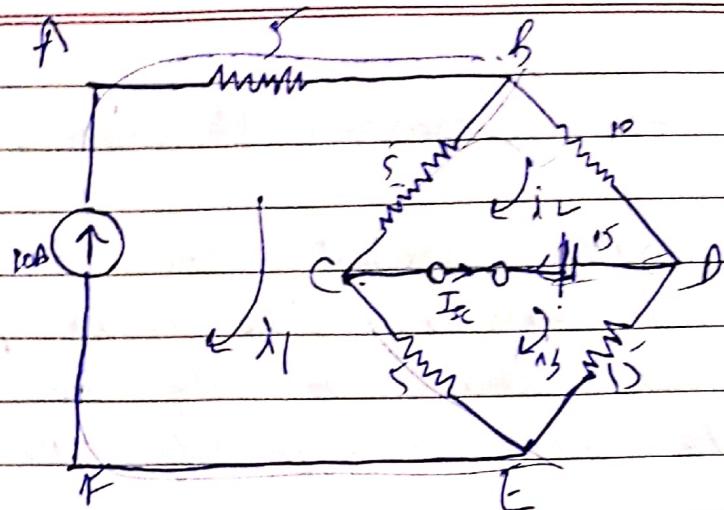
$$R_{in} = R_{AB} = \frac{15 \times 20}{35} \parallel (15 \parallel 20)$$



KVL in mesh ABCFEFA



$$i_1 = 10 \text{ A.}$$

KVL in mesh BCDB,

$$-5(i_1 - i_2) - 10i_2 + 15 = 0.$$

KVL in mesh COEC


$$-15i_3 - 5(i_3 - i_1) - 15 = 0$$

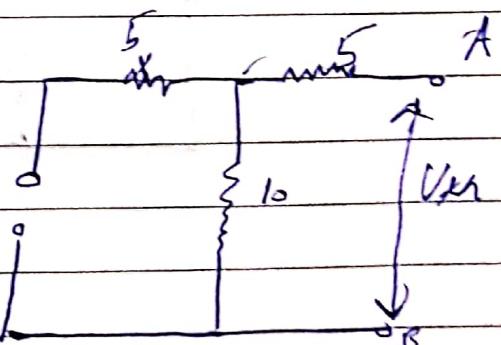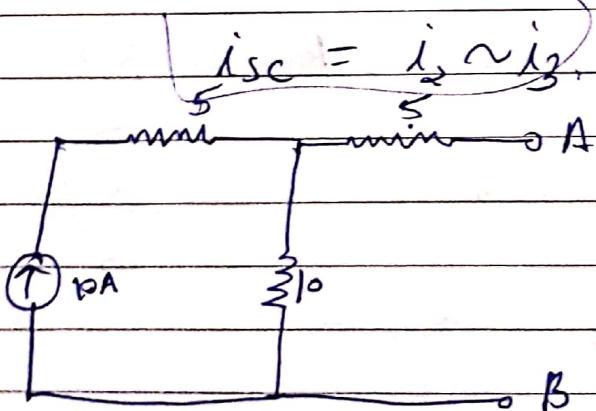

Thevenin circuit eq.

$$R_{AB} = R_{th} = 15.$$

KCL at node 1,

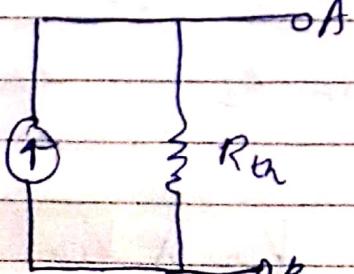


$$\frac{V_1}{10} - 10 = 0$$


$$V_1 = 100 \text{ V.}$$
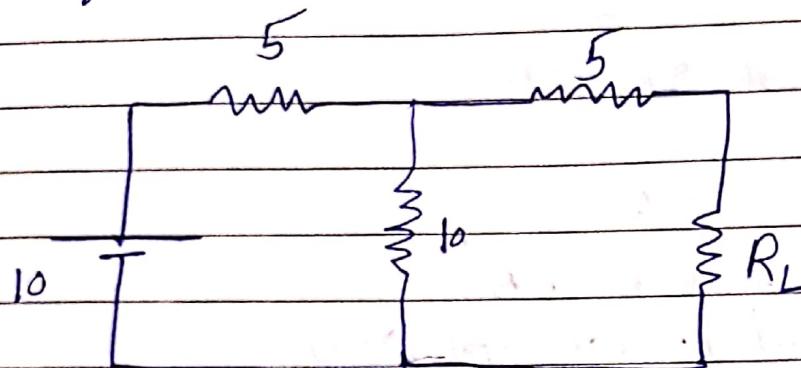
## \* Maximum power transfer theorem:

→ States that in any circuit the load resistance will consume the max. power when value of that node resistance is equal to the Thévenin resistance of the circuit.




As per rule,  $R_L = R_{th}$

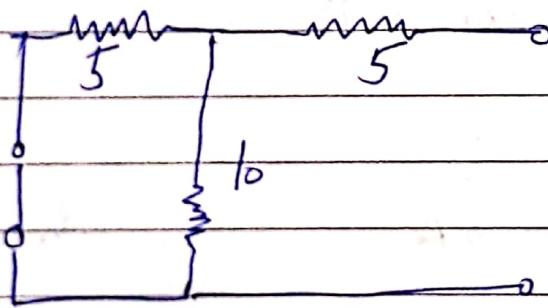

$$R_{th} = \frac{15}{125} + 5 - \frac{15}{15}$$

$$R_L = \frac{125}{15} \Omega$$


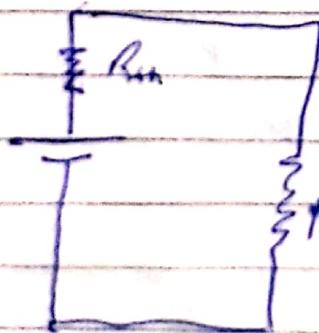


$$I = \frac{V_{th}}{R_{th} + R_L} = \frac{V_{th}}{2R_{th}}$$

$$P = V \times I = V_{th} \times \underline{V_{th}}$$

$$\text{also } P = I^2 R = \left(\frac{V_{th}}{2R_{th}}\right)^2 \cdot R_{th} = \frac{V_{th}^2}{4R_{th}}$$

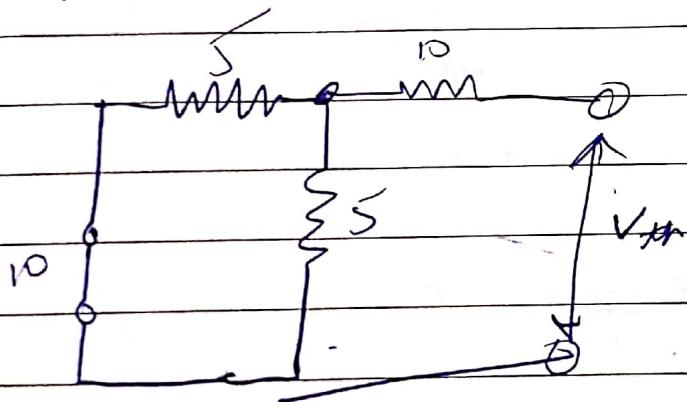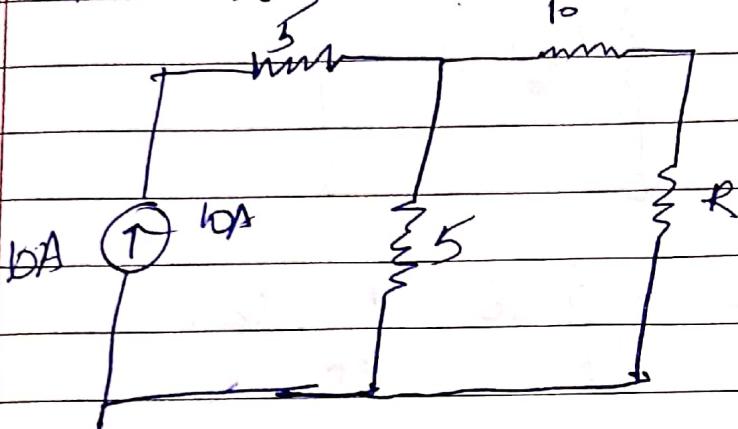Q) For a given circuit determine the value of  $R$  for which it will consume max. power & also determine the mag. of that power.




$$R = R_{th} = 15\Omega$$

$$\frac{V_1}{5} - 10 = 0$$

$$V_1 = 50V_1 = V_{th}$$

$$P_{max} = \frac{50^2}{4 \times 15}$$

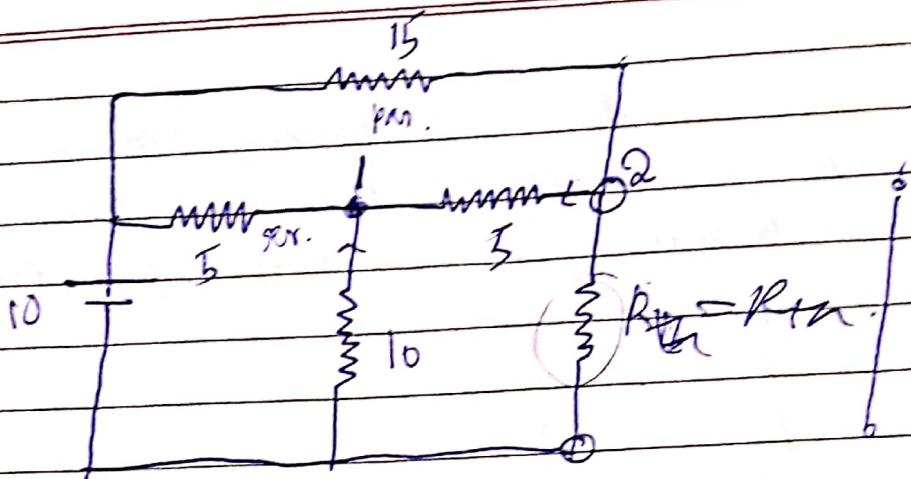

$$R_L = R_{th} = \frac{15}{\frac{10}{5} + \frac{10}{5}} = \frac{15}{4}$$


$$\therefore R_L = \frac{15}{4} \Omega$$

By KCL at Node 1,

$$\frac{V_1 - 10}{5} + \frac{V_1}{10} + \frac{V_1 - V_2}{5} = 0$$

KCL at node 2,

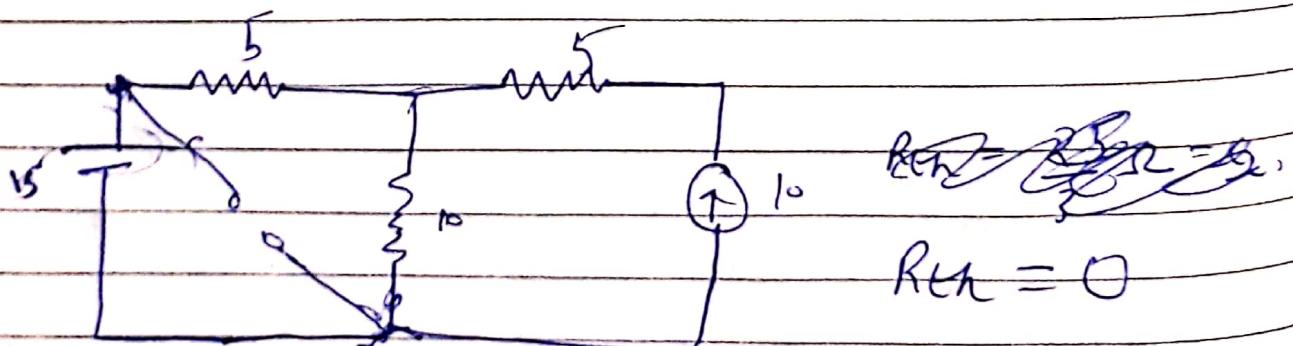
$$\frac{V_2 - 10}{15} + \frac{V_2 - V_1}{5} = 0$$



$$V_{th} = V_{AB} = 15$$

→ Superposition Theorem: any linear network consists of components contains current

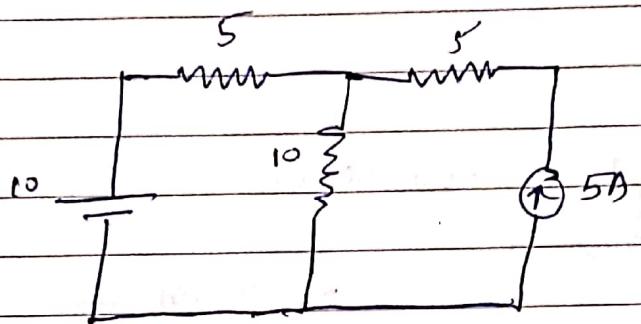→ Consider a 10V source. Replace 5A current source by internal resistance i.e.  $\infty$



$$i = 10 \text{ A.}, \text{ upward to downward.}$$

Thévenin  
Theorem  
Source  
Substitution  
Monday.

Laplace transform:

$$\Rightarrow f(t) = \int_0^\infty e^{-st} f(t) dt$$

$$\Rightarrow L(1) = \frac{1}{s} \quad L(10) = \frac{10}{s}, \quad L(15) = \frac{15}{s}$$

$$L(e^{at}) = \int_0^\infty e^{-st} \cdot e^{at} \cdot dt = \frac{1}{s-a}$$


$$L(n) = \frac{n}{s}$$

~~Wrote few of error  
in test~~

$$\text{or } V_i = L \cdot \frac{dV}{dt}$$

~~experiment~~

→ Verification of Ohm's law:

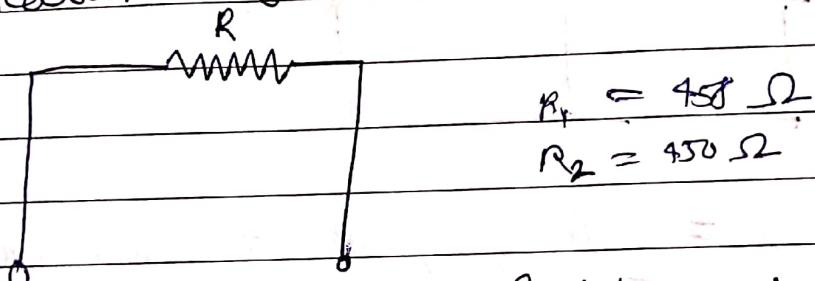

- ① Measure value of Resistance by multimeter.
- ② connect one resistance breadboard
- ③ Give DC supply to the circuit.

1)  $V = 10V$

$R = 322 \Omega$

$I = \frac{10}{322} = 0.0310A$

Actual value of  $I = 0.04A$

3)  $V = 20V$

$R = 322\Omega$

$I = 0.0621A$

Actual value = 0.07A

2)  $V = 15V$

$R = 322\Omega$

$I = \frac{15}{322} = 0.046A$

Actual value = 0.05A

4)  $V = 25V$

$I = 0.077A$

Actual value = 0.08A

5)  $V = 30V$



$I = 0.09A$

Actual value = 0.1A

\* Verification of KVL:

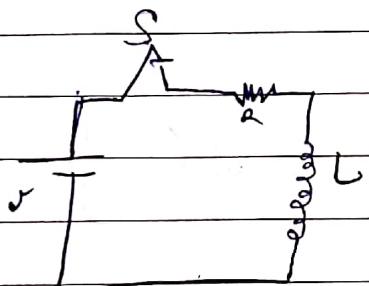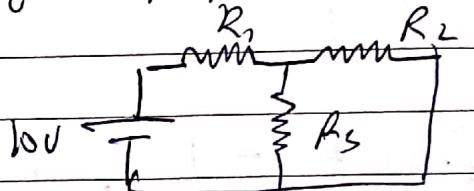- 1) Connect all three resistance in series
- 2) give 10V supply.
- 3) measure voltage drop across all resistors.

\* Verification of superposition Theorem:



$$i(t) = \frac{V'}{R} = \frac{V'e^{-R/Lt}}{R}$$

$$V_L(t) = V e^{-R/Lt}$$

Q. A series RL circuit is feded by voltage source 100V with help of switch. The switch is closed at  $t=0$ . Determine the current

- a) Find exp.
- b) Voltage across inductor exp.

c) Time constant

Assume  $R = 10\Omega$ ,  $I = 1\text{mA}$ .


$$V = 100V$$

$$i(t) = \frac{V}{R} (1 - e^{-R/Lt}) = \frac{100}{10} (1 - e^{-10/1 \times 10^{-3} t})$$

$$V_L(t) = V e^{-R/Lt}$$

$$Z = \frac{L}{R} = \frac{1 \times 10^{-3}}{10} \text{ sec.}$$

RC circuit

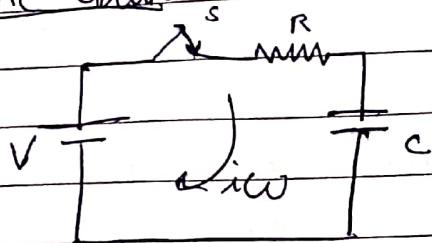

$$V = R i(t) + \frac{1}{C} \int i(t) dt.$$

Take Laplace

$$\frac{V}{s} = R i(s) + \frac{1}{C} \left[ \frac{i(s)}{s} - V_L(0^-) \right]$$

$$V_L(0^+) = 0,$$

$$i(s) = \frac{V}{s(R + \frac{1}{Cs})}$$

$$i(s) = \frac{V}{R(s + \frac{1}{RC})}$$

Take inverse Laplace

$$i(t) = \frac{V}{R} e^{-t/RC}$$

$$V_L(t) = \frac{1}{C} \int_0^t i(t) dt$$

$$= \frac{1}{C} \int_0^t \frac{V}{R} e^{-t/RC} dt$$

$$= \frac{V}{R} \left[ \frac{e^{-t/k_c}}{1/k_c} \right]_0^t$$

$$= V [1 - e^{-t/k_c}]$$

$$\rightarrow i(t) = \frac{V e^{-t/k_c}}{R}$$

$$\rightarrow V_C(t) = V [1 - e^{-t/k_c}]$$

$\Rightarrow$  AC circuit Analysis:

$$V(t), V = V_m \sin \omega t,$$

- 1) Peak Value
- 2) Average
- 3) RMS value
- 4) Inst. value.

Q. PT for AC cycle avg value is "

$$\text{Ans} \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T V^2(t) dt} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t dt} = \frac{V_m}{\sqrt{2}}$$

$$\frac{V_m}{\sqrt{2\pi}} \sqrt{\int_0^{2\pi} \left( \frac{1 - \cos 2\omega t}{2} \right) dt} = \frac{V_m}{\sqrt{2\pi}} \sqrt{\int_0^{2\pi} \left[ \frac{1}{2} \omega t - \frac{1}{2} \frac{\sin 2\omega t}{2} \right] dt}$$

$$= \frac{V_m}{\sqrt{2\pi}} \sqrt{\frac{\pi}{2}} = \frac{V_m}{\sqrt{a}}$$


$$= \frac{V_m}{\sqrt{2} \sqrt{a}} = \frac{V_m}{\sqrt{a}}$$

⇒ form factor =  $\frac{\text{RMS}}{\text{Average}}$

→ AC circuit analysis:

$$V(t) = i(t)R$$

Capacitive circuit

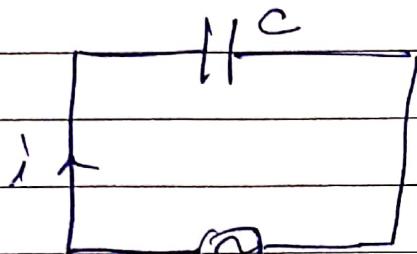

$$V = V_m \sin \omega t$$

$$V(t) = V_m \sin \omega t$$



$$i(t) = C \frac{d(V/t)}{dt}$$

$$= C \frac{d(V_m \sin \omega t)}{dt}$$

$$= V_m C \cos \omega t (\text{A})$$

$$= \frac{V_m}{X_C} \cos \omega t$$

$$\therefore I_m = \frac{V_m}{X_C}$$

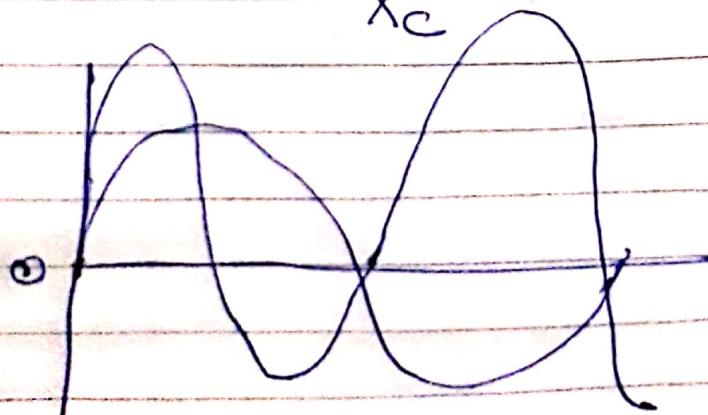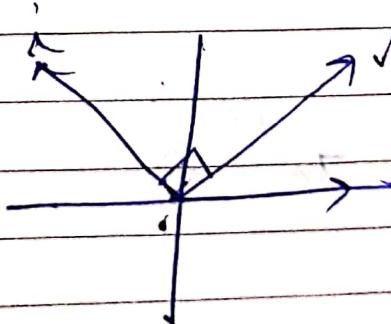

Q. A  $10\Omega$  resistance is feeded by AC source of  $200V, 50Hz$  freq. Determine

- i)  $V$
- ii)  $I$
- iii)  $V_{rms}$ ;  $I_{rms}$
- iv)  $\phi$ ; Power factor angle
- v) Power factor
- vi) phasor & time diagrams.

$$V = V_m \sin \omega t$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V = 200\sqrt{2} \sin 50 \times 3.14 \times t \quad 200\sqrt{2} = V_m$$

$$V = V_m \sin \omega t$$

$$V_m = 200$$

$$\omega = 50 \text{ rad/s}$$

$$i = \frac{V_m \sin \omega t}{R}$$


$$I_{rms} = \frac{I_m}{\sqrt{2}}$$


$$= 200\sqrt{2} \sin 2\pi ft$$

$$\phi = 0^\circ$$

$$i = 20\sqrt{2} \sin 50 \times 3.14 \times t$$

$$P_F = V I \cos \phi$$

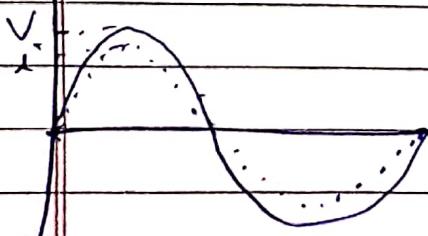

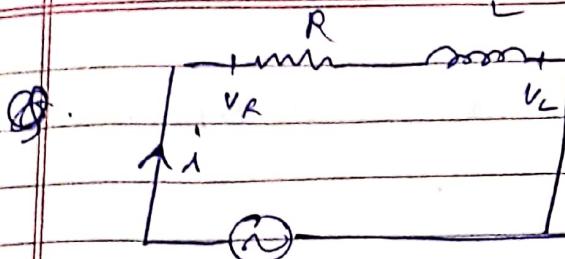

RL circuit analysis:

$$V_R = iR$$

$$V_L = iX_L \rightarrow V^2 = V_R^2 + V_L^2$$

$$\frac{V^2}{i^2} = R^2 + X_L^2$$

$$Z^2 = R^2 + X_L^2$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$i(t) = \frac{V(t)}{Z} = \frac{V_m \sin(\omega t - \phi)}{Z}$$

$$i(t) = \frac{V_m \sin(\omega t - \phi)}{\sqrt{R^2 + X_L^2}}$$

$$\tan \phi = \frac{V_L}{V_R}$$

$$= \frac{iX_L}{iR}$$

$$\therefore \phi = \tan^{-1}\left(\frac{X_L}{R}\right)$$

Q) \* Types of Power:

→ Active power:  $VI \cos \phi = P$  (watt)→ Reactive power:  $VI \sin \phi = Q$  (volt-Amper)→ Apparent power (Active power  $\times$  reactive power)  $S$ 

$$S = \sqrt{P^2 + Q^2}$$



Q. A series RL circuit is fed by AC source of 200V, 50Hz

$$R = 10$$

$$L = 1 \text{ mH}$$

$$\omega = 2\pi f \theta.$$

Determine:

- 1) Exp. of V,
- 2) Impedance
- 3) Phase angle
- 4) Current expression
- 5) Active, reactive & apparent power.

$$V_s = 200\sqrt{2} \sin(2\pi 50t)$$

$$X_L = 2\pi f L$$

$$Z = \sqrt{R^2 + X_L^2}$$


$$X_C = \frac{1}{2\pi f C}$$

$$= \sqrt{10^2 + (2\pi 3.14 \times 50 \times 10^{-3})^2}$$

$$\phi = \tan^{-1}\left(\frac{X_L}{R}\right) = \tan^{-1}\left(\frac{2\pi 3.14 \times 50 \times 10^{-3}}{10}\right)$$

$$\rightarrow i = \frac{V_m \sin(\omega t - \phi)}{Z}$$

$\Rightarrow$  Analysis of RC circuit:

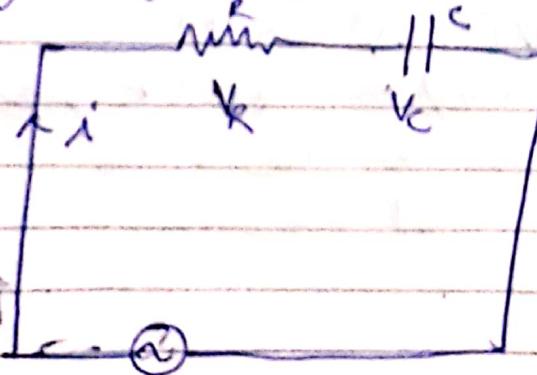

$$V_R = iR$$

$$V_C = iX_C$$

$$V = \sqrt{V_R^2 + V_C^2}$$

$$V^2 = \cancel{P} \frac{i^2 R^2 + i^2 X_C^2}{i^2 R^2 + i^2 X_C^2}$$

$$Z = \sqrt{R^2 + X_C^2}$$


$$i(t) = \frac{V(t)}{Z}$$

$$= \frac{V_m \sin(\omega t + \phi)}{\sqrt{R^2 + X_C^2}}$$

$$= \frac{V_m}{\sqrt{R^2 + X_C^2}} \sin(\omega t + \phi)$$

$$\phi = \tan^{-1} \left( \frac{X_C}{R} \right)$$

$$P = V(t) i(t)$$

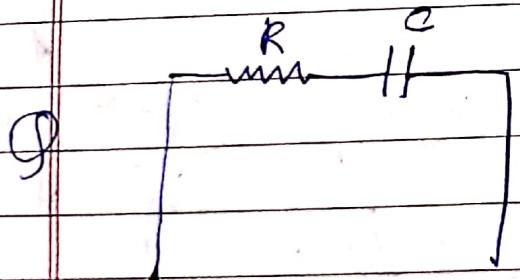

A series RC circuit is fed 200V AC & 50Hz freq.

Determine the following:

a) exp. for supply voltage

$\frac{1}{50} \times 10^3$

$$a) V = 200\sqrt{2} \sin 2 \times 3.14 \times 50 \times t$$

$$b) I = \frac{200\sqrt{2}}{100} = 20\sqrt{2} \sin 2 \times 3.14 \times 50 \times t$$

$$c) Z = \sqrt{100 + }$$


$$\phi = \tan^{-1} \left( \frac{X_C}{R} \right)$$

$$P = VI \cos \phi$$

$$\Phi = VI \sin \phi$$

$$S = \sqrt{P^2 + \Phi^2}$$

$\Rightarrow$  Series RLC circuit:

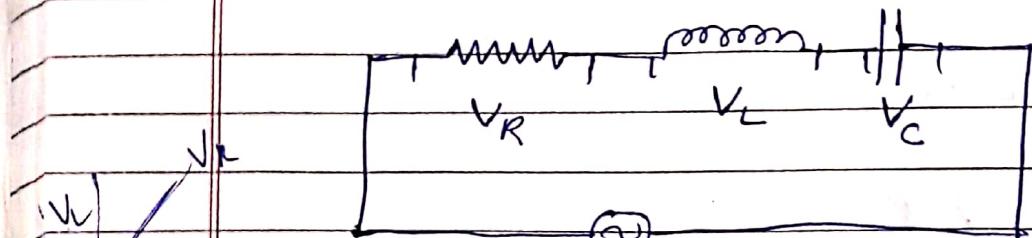


$$V = V_m \sin \omega t$$


$$V_R = iR$$

$$V_L = iX_L$$

$$V_C = iX_C$$

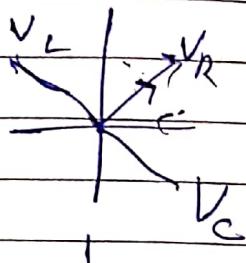

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

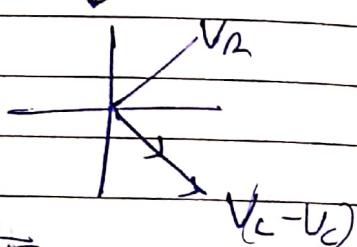

$$\therefore Z = \sqrt{R^2 + (X_L - X_C)^2}$$


$$X_C > X_L$$

$$(+\phi)$$

$$X_L > X_C$$

$$(-\phi)$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

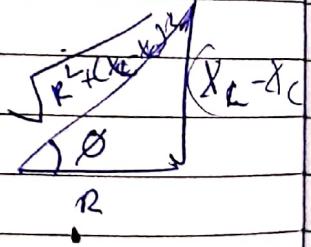

$$i(t) = \frac{V(t)}{Z} \sin(\omega t + \phi)$$

$$\tan \phi = \frac{X_L - X_C}{R}$$

$$V = 100 \sin 20t$$

$$mH = 10^{-3} H$$

$$\mu F = 10^{-6} F$$


$$Z = \sqrt{i^2 + (20 \times 10^{-3})^2}$$

$$\text{Ans } \phi = \tan^{-1} \frac{X_L - X_C}{R}$$

$$i = \frac{V(t)}{Z} \sin(\omega t + \phi)$$

$$= \frac{100}{Z} \sin(20t + \phi)$$

## → Series Resonance:

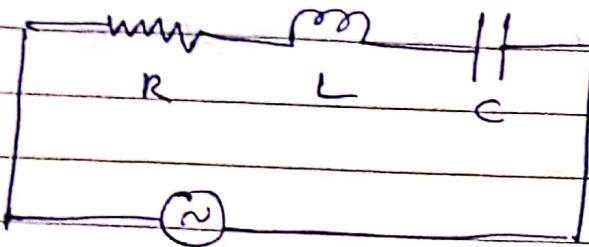

$$V(t) = V_m \sin \omega t$$

$$X_L = \omega L$$

$$X_C = \frac{1}{\omega C}$$

$$X_C = X_L$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 LC = 1$$

$$\omega^2 = \frac{1}{LC}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L = X_C$$

$$\therefore Z = R$$

1) Impedance will be minimum

2) Current will be max.

3) Resistive circuit.


4) Voltage & current will be in same phase.

5) Phase angle 0

6) PF will be unity



Power factor ✓

## \* Harmonics:

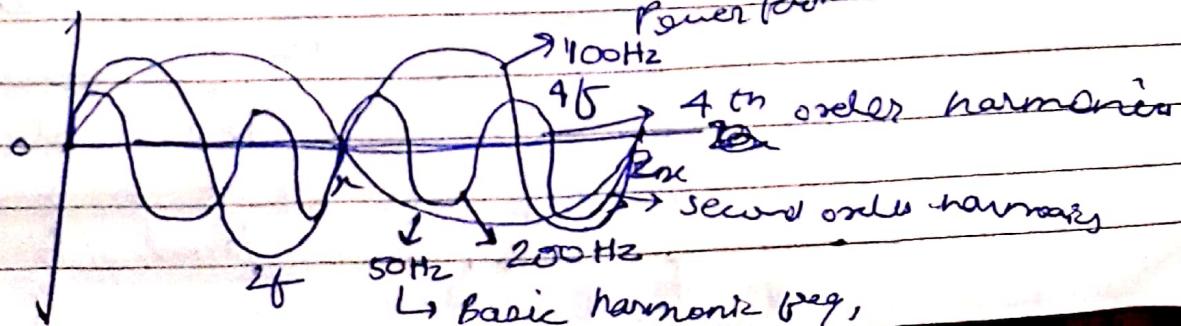

$\Rightarrow$  Harmonics: Sineoidal signals whose frequency different than base ~~frequency~~ signal.

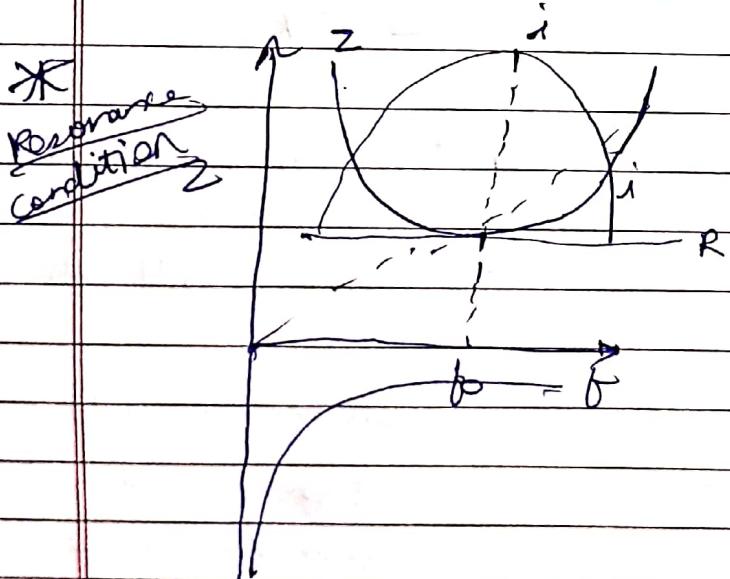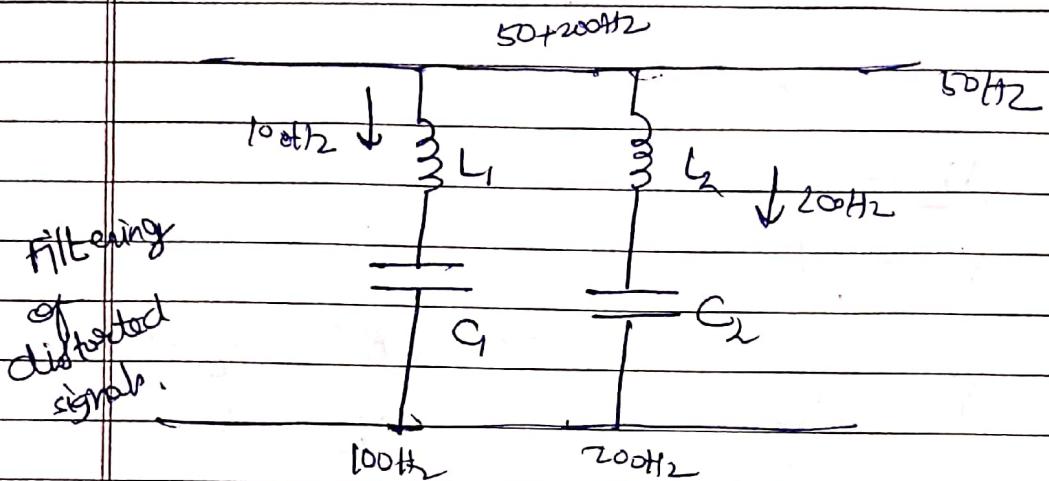
$$50\text{Hz} + 100\text{Hz} + 200\text{Hz}$$



$$X_L = \omega L$$

$$= 2\pi f L$$

\* Half Power frequencies,

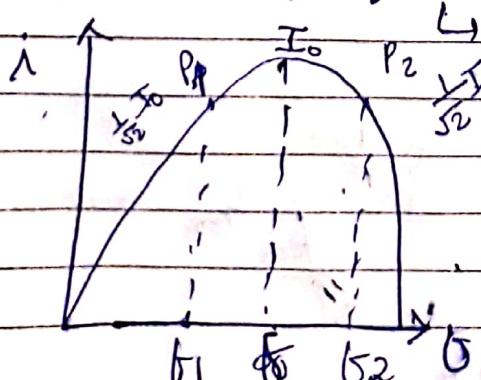

at which current will be  $\frac{1}{\sqrt{2}}$  times the resonance current.

These pts are called

$$\text{Bandwidth} = f_2 - f_1$$

$$(I) f_0 = \left( \frac{V}{\sqrt{R^2 + (x_L - x_C)^2}} \right)^2 R = \frac{1}{2} \frac{V^2 R}{2} = \frac{1}{2} \left( \frac{V}{R} \right)^2 R$$

(at half power frequency)

$$\frac{V^2}{R^2 + (x_L - x_C)^2} \cdot R = \frac{1}{2} \frac{V^2}{R}$$

$$R^2 + (x_L - x_C)^2 = 2R^2$$

$$x_L - x_C = R^2$$

$$\boxed{R = x_L - x_C}$$

$$\omega L - \frac{1}{\omega C} = R$$

$$\omega^2 LC - \omega CR - 1 = 0$$

$$LC \left( \omega^2 - \frac{\omega CR - 1}{LC} \right) = 0$$

$$\omega^2 - \frac{\omega R}{L} - \frac{1}{LC} = 0$$

$$\omega_1 = \frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} + 4 \times \frac{1}{LC}}$$

$\frac{2 \times 1}{}$

$$\rightarrow \omega_1 = \frac{R}{2L} + \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$\rightarrow \omega_2 = \frac{R}{2L} - \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$f_1 = \frac{R}{4\pi L} + \frac{1}{2\pi} \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$


$$f_2 = \frac{R}{4\pi L} - \frac{1}{2\pi} \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

$$\text{Bandwidth} = f_2 - f_1$$


$$= -\frac{1}{\pi} \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

## Unit 2: Magnetic Circuit.

magnetic circuit

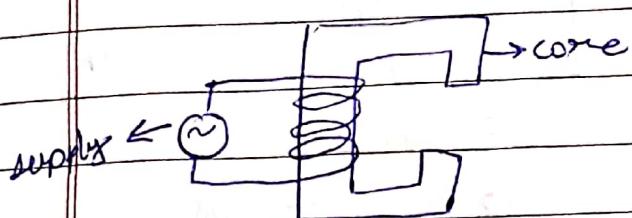

Elec. circuit

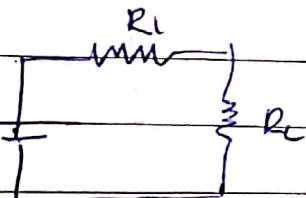

EmF

- Current
- Resistance
- Elec. field intensity
- Conductivity

MMF  
(magnetomotive force)


magnetic flux

Reluctance

magnetic field intensity

→ Faraday: 1) Change in flux generates emf in a coil

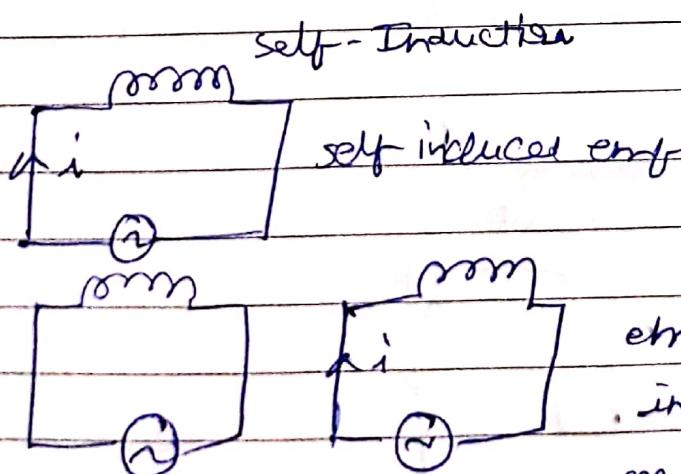→ 2) Induced emf  $= -\frac{d\phi}{dt} = -N \frac{d\phi}{L_{\text{turns}} dt}$




emf induced due to current in one coil.

mutual inductance  $\rightarrow$  magnetic material  
Reluctance  $\rightarrow$  material oppose the flow to flux


⇒ Types of magnetic circuit:

- 1) Series
- 2) parallel



→ Series magnetic circuit:

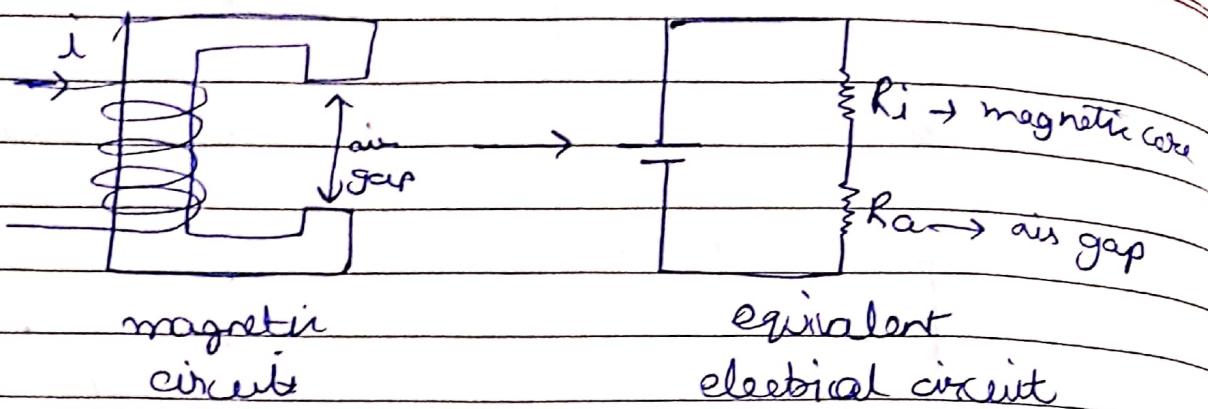


→ Parallel magnetic circuit:

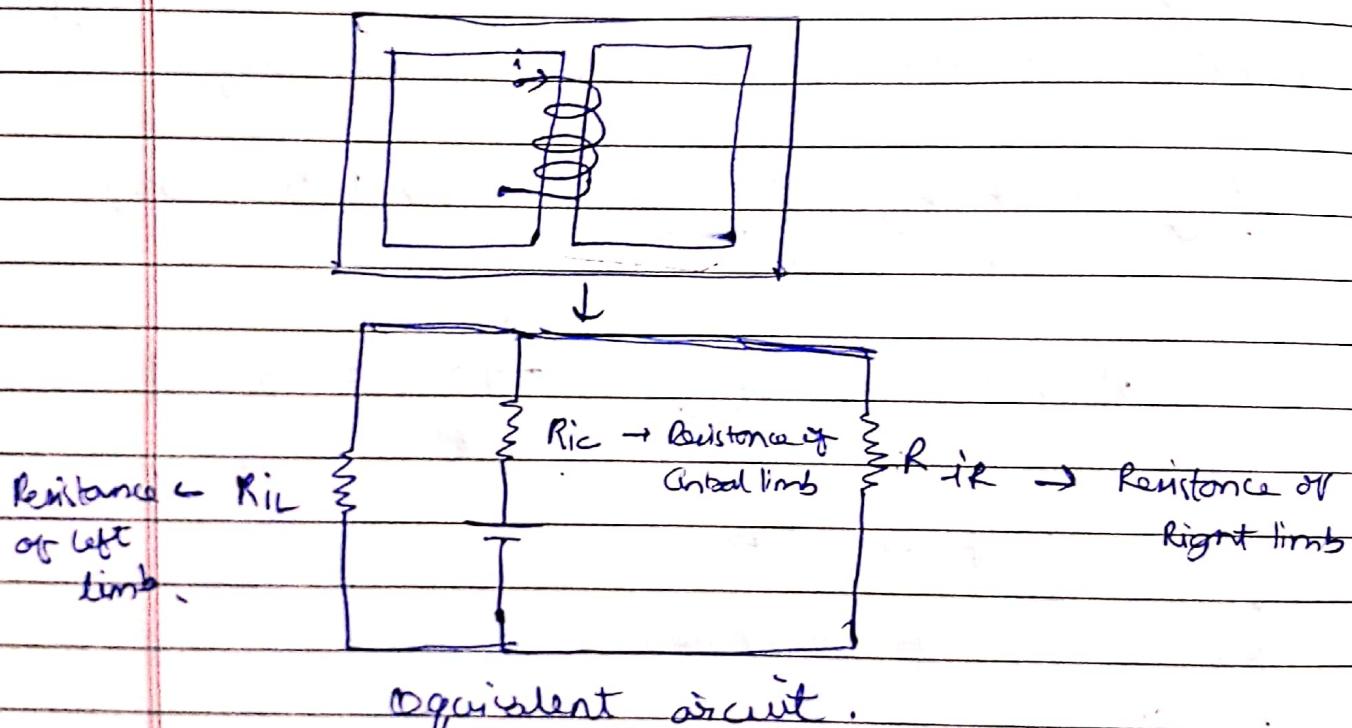

e.g.: 1)

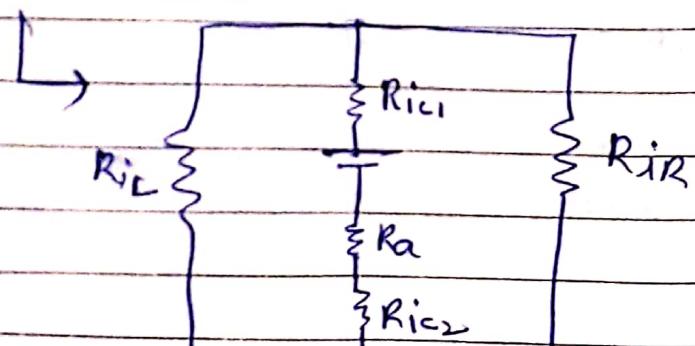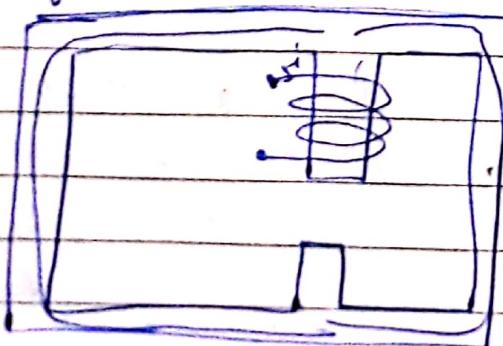


2)

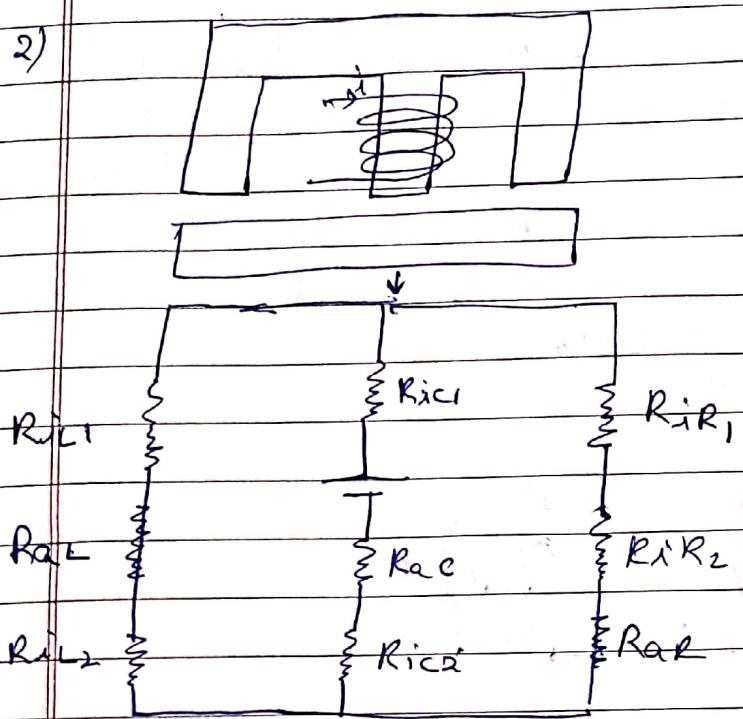

→ magnetically coupled coils:

~~Dot convention rule~~: Dot convention rule helps to determine the polarity of induced emf in magnetically coupled coil.

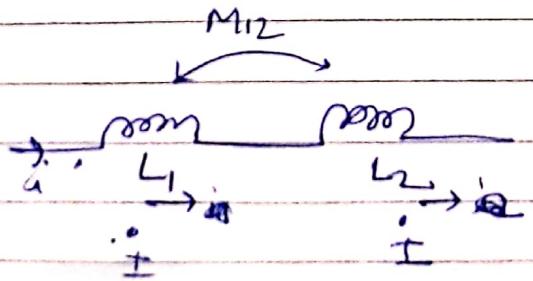As per rule, a dot will be placed at that end of the coil which are having similar polarity & induced emf.



away from dot  
+  
towards  
→ one away one towards  
-

$$e_{11} = -L_1 \frac{di}{dt}$$

$$e_{22} = -L_2 \frac{di}{dt}$$

$$e_{12} = -M_{12} \frac{di}{dt}$$



$$e_{21} = -M_{21} \frac{di}{dt}$$

Total emf,

$$e = -L_1 \frac{di}{dt} + -m_{12} \frac{di}{dt} - L_2 \frac{di}{dt} + -m_{21} \frac{di}{dt}$$



$$= -(L_1 + L_2 + 2m_{12}) \cdot \frac{di}{dt}$$

$\therefore$  equivalent Inductance

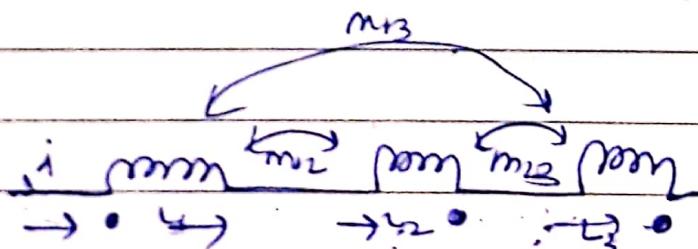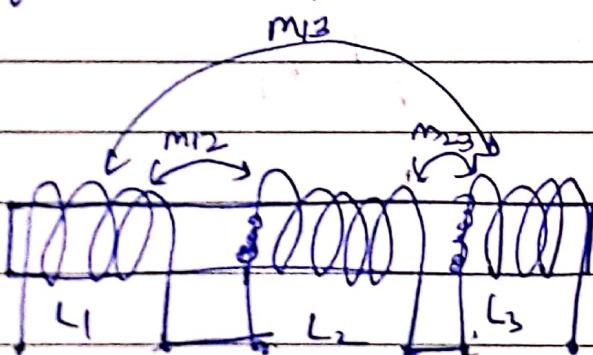


$$-\frac{L_1}{\partial t} \frac{di}{dt} - \left( -m_{12} \frac{di}{dt} \right) \left( -m_{23} \frac{di}{dt} \right)$$
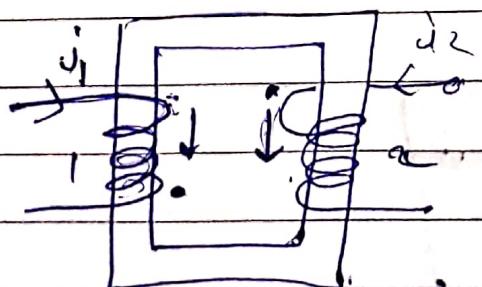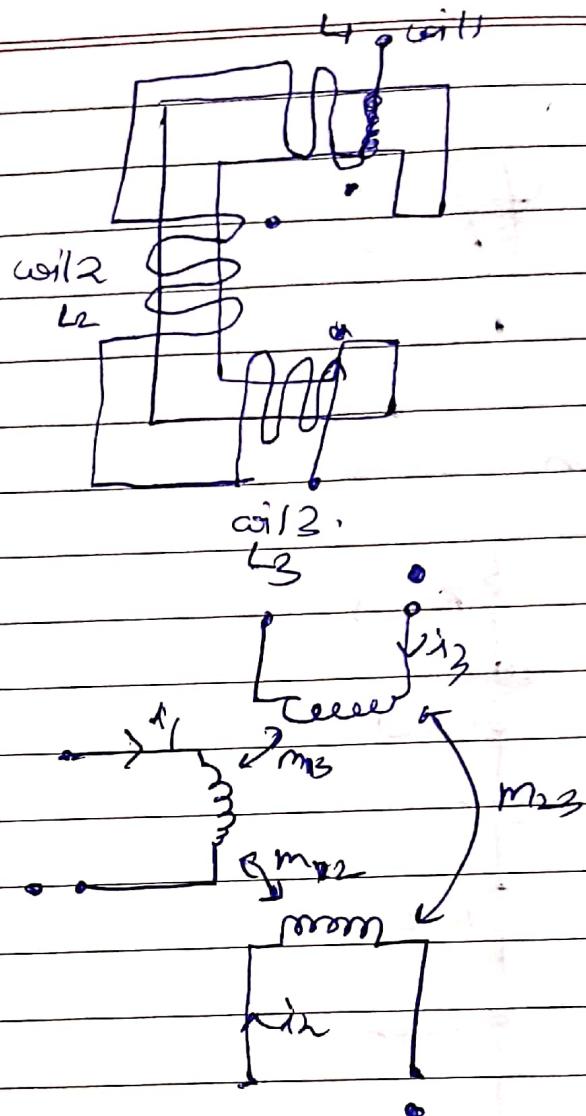
$$-L_2 \frac{di}{dt} - \left( m_{23} \frac{di}{dt} \right)$$





$$e_1 = -L_1 \frac{d\mathbf{j}_1}{dt} - \left( -m_{12} \frac{d\mathbf{j}_2}{dt} \right)$$
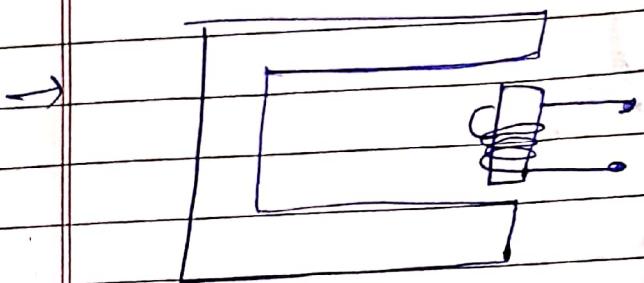
$$e_2 = -L_2 \frac{d\mathbf{j}_2}{dt} - \left( -m_{21} \frac{d\mathbf{j}_1}{dt} \right).$$




→ elec. equivalent circuit.

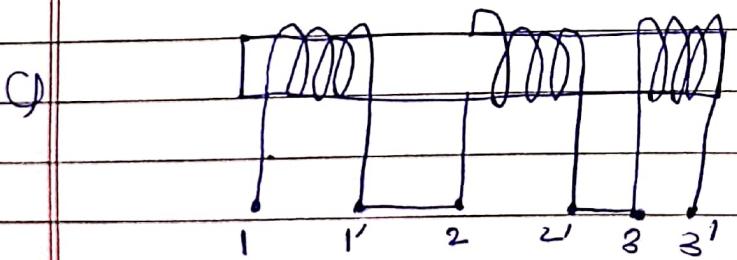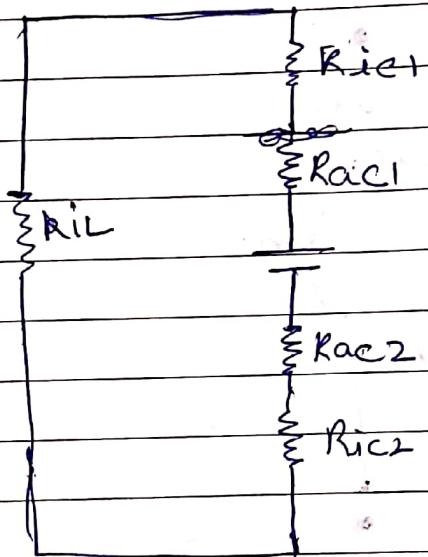


Series

a)  $i' - 2 \quad 2i - 3$

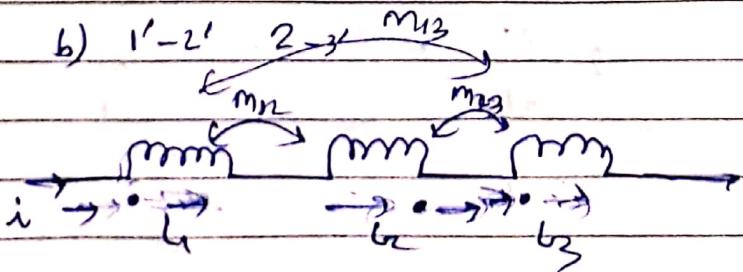

$$\begin{aligned}
 & -L_1 \frac{di}{dt} + \left( -m_{12} \cdot \frac{di}{dt} \right) + \left( -m_{13} \cdot \frac{di}{dt} \right) \\
 & -L_2 \cdot \frac{di}{dt} + \left( -m_{23} \cdot \frac{di}{dt} \right)
 \end{aligned}$$
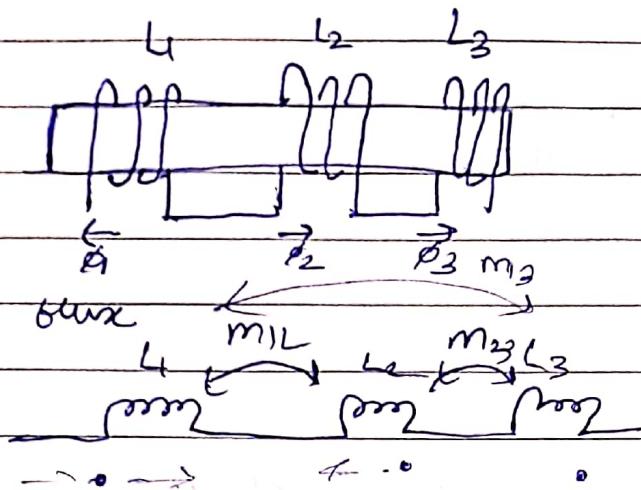
$$-\frac{L_3 \cdot di}{dt} - \left( -m_{13} \frac{di}{dt} \right)$$



$$\Sigma = -L_1 \frac{di}{dt} - \left( m_{12} \frac{di}{dt} \right) + \left( -m_{13} \frac{di}{dt} \right)$$

$$-L_2 \frac{di}{dt} - \left( -m_{12} \frac{di}{dt} \right) - m_{13} \frac{di}{dt}$$

$$-L_3 \frac{di}{dt} - m_{23} \frac{di}{dt} + m_{13} \frac{di}{dt}$$

\* Magnetic flux density is flux per unit area.

$$B = \frac{\Phi}{A} = \text{weber/m}^2$$

magnetic field intensity

$$H = \frac{Ni}{L} = \frac{mmf}{length} = \frac{F}{L}$$

$$\Phi = BA$$

$$= \mu H A$$

$$= \mu \frac{Ni}{L} A$$


$$= \frac{Ni}{\frac{L}{\mu A}}$$

$$= \frac{Ni}{S}$$

$$\text{Resistance} = \frac{S \cdot l}{\alpha}$$

$$\text{Reluctance} = \frac{l}{\mu A}$$

$$\Phi = \text{mmf} \cdot S$$

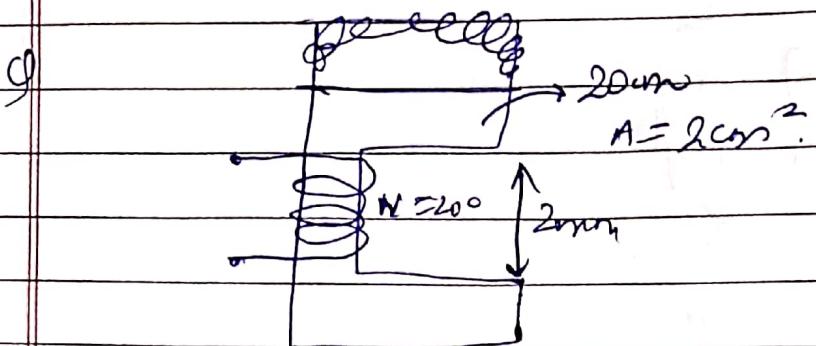

A rectangular core made up of soft iron having  $\mu = 2000$  is excited by a magnetic coil with  $N = 200$  &  $I = 5\text{A}$ . The mean length of the flux in the core is  $l = 20\text{cm}$ . If the rectangular core is having an air gap of  $2\text{mm}$ . Then determine the flux developed in a magnetic core & air gap. Also the area of the core is  $2\text{cm}^2$ .

$$\Phi = Ni \cdot S$$

$$= \text{mmf} \cdot S$$


$$\text{mmf} = NI = 200 \times 5 = 1000\text{AT}$$

$$S_{\text{air}} = \frac{l_a}{\mu_r H_0} = \frac{(20 - 0.2) \times 10^{-2}}{4 \times 10^{-7} \times 2000 \times 2 \times 10^{-4}} \text{m}^2$$

*per. of air =  $2 \times 10^{-2}$*

$$S_a = \frac{l_a}{H_0 A} = \frac{0.2 \times 10^{-2}}{4 \times 10^{-7} \times 2 \times 10^{-4}}$$

$$S = S_i + S_a$$

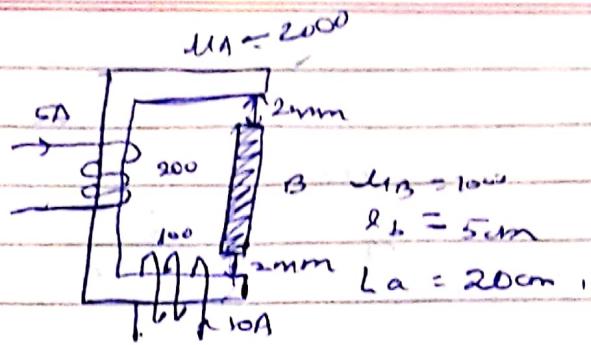

$$\begin{aligned}
 \text{MMF} &= N_1 I_1 + N_2 I_2 \\
 &= 200 \times 5 + 100 \times 10 \\
 &= 2000 \text{ AT}
 \end{aligned}$$

$$\begin{aligned}
 S_a &= \frac{I_a}{\mu_0 M_B} A & A &= 200 \text{ cm}^2 \\
 &= \frac{200 \times 10^{-2}}{4 \times 10^{-7} \times 2000 \times 2 \times 10^{-4}}
 \end{aligned}$$

$$S_b = \frac{l_b}{\mu_0 M_B} A = \frac{5 \times 10^{-2}}{4 \times 10^{-7} \times 1000 \times 2 \times 10^{-4}}$$

$$S_{air} = \frac{I_a}{\mu_0 A} = \frac{200 \times 2 \times 10^{-2}}{4 \times 10^{-7} \times 2 \times 10^{-4}}$$

$$S = S_a + S_b + S_{air}$$

$$\Phi = \frac{E}{S}$$

Q) A circular ring air. by mag. coil having  $N = 200$  &  $i = 10A$ , air gap of 1mm. If area of A =  $2 \text{ cm}^2$  & mean length of flux is 20cm. Determine flux per unit magnetic core,  $\mu_r = 1000$

$$mmf = Ni$$

$$= 200 \times 10 = 2000 \text{ AT}$$


$$S_i = \frac{(20 - 0.1) \times 10^{-2}}{4 \times 10^{-7} \times 1000 \times 2 \times 10^{-4}} \text{ weber} \rightarrow l_i$$

$$S_a = \frac{0.1 \times 10^{-2}}{4 \times 10^{-7} \times 2 \times 10^{-4}} = \frac{l_a}{\mu_0 \text{ A}}$$

$$S = S_i + S_a$$

$$\emptyset = \frac{F}{S}$$

## Unit 3: Electrical Machines.

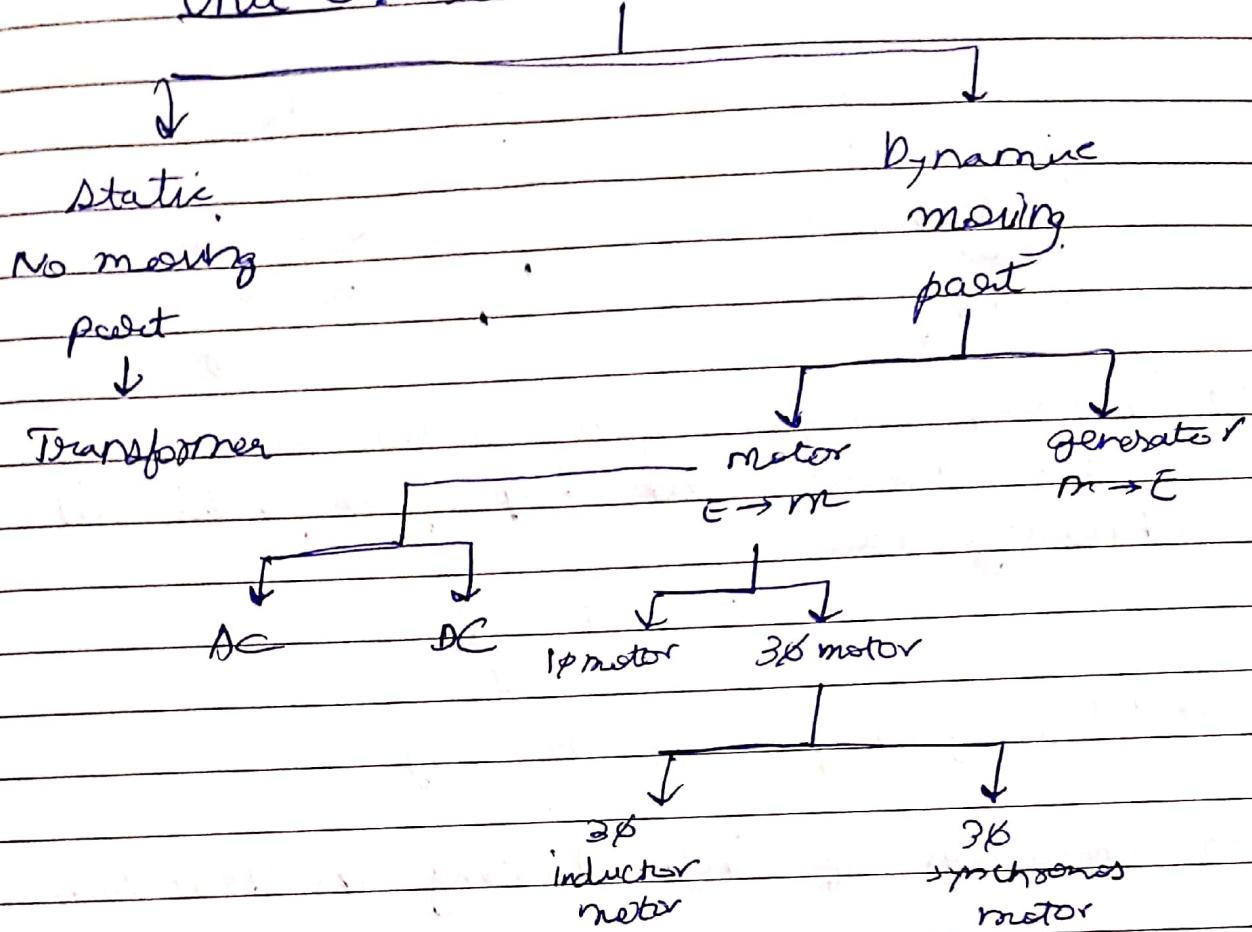


### → Transformer :

- \* Static m/c
- \* It is used to transfer power from one elec. circuit to other elec. circuit which are electrically isolated but magnetically coupled.
- \* It is used to transfer power of different voltage / I maintaining power & freq. constant.
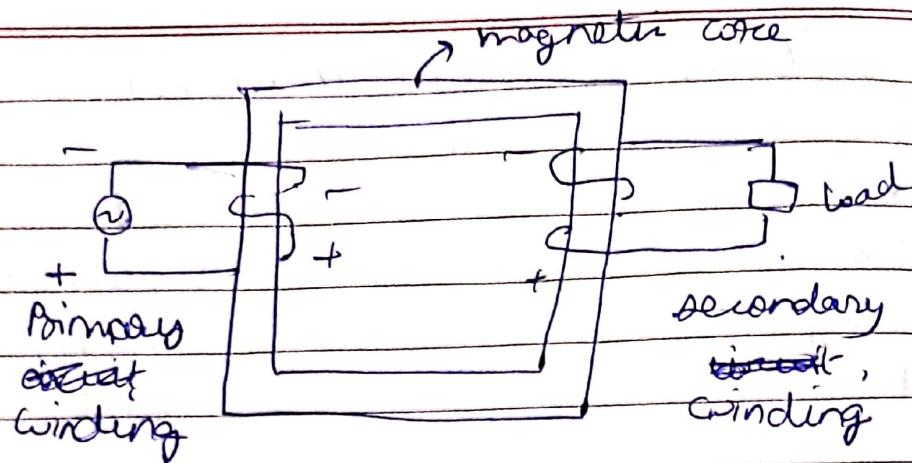
### → Winding loss

- \* highest efficiency machine (90 - 95%).



→ Operating principle: power shifted from primary  
- sec. circuit with help of magnetic coil  
(Faraday's law)

$$e = -N \frac{d\phi}{dt}$$

→ Polarity keeps on changing.

→ Expression of induced emf in Transformer:

As per Faraday's second law,

$$e = -N \cdot d\phi$$

Change  $d\phi$   
in flux between 0 to  $T\pi$ .  
 $d\phi = \phi_{max} - 0$

Change in time,

$$dT = T/4 - 0$$

Q. Self emf induced in primary coil,

$$E_1 = -N_1 \frac{d\phi}{dt}$$

$$= -N_1 \frac{\phi_{max}}{T/4}$$

$$E_1 = -4 N_1 \phi_{max}$$

Ques. Mutual inductor induced emf in secondary coil,

$$E_2 = -N_2 \frac{d\phi}{dt}$$

$$= -N_2 \frac{\phi_{\max}}{T/4}$$

$$E_2 = -4N_2 \phi_{\max} f$$

rms value of induced emf

$$E_{2\text{rms}} = -4 \phi_{\max} N_2 f \times 1.11$$

$$= -4.44 N_2 \phi_{\max} f$$

$$E_{2\text{rms}} = -4.44 N_2 \phi_{\max} f$$

Q.

$$\begin{array}{c} E \propto N \\ \boxed{\frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1} = k} \\ E \propto \frac{1}{L} \end{array}$$

Transformation ratio.

→ Operation of Transformer:


- \* High Voltage winding is made up of thin wire.
- \* Low voltage winding is made up of thick wire.

(a) No load operation

(b) Load operation.

connected.

→ No load to secondary side.

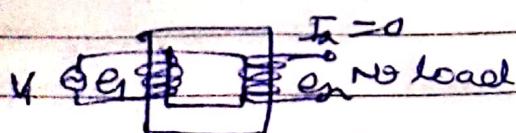

→ No load operation



No load :

Current flowing in primary winding  
flux developed.

$e_1 \ e_2$

2 KVA 200/100V


$$I_1 = \frac{2 \times 1000}{200} = 10 \text{ A}$$

2 KVA 100/200V


$$I_2 = \frac{2 \times 1000}{100} = 20 \text{ A}$$

$I_o$  Working magnetization  
 $I_w$  watt.  $I_m$  wattless





→ Phasor diagram :

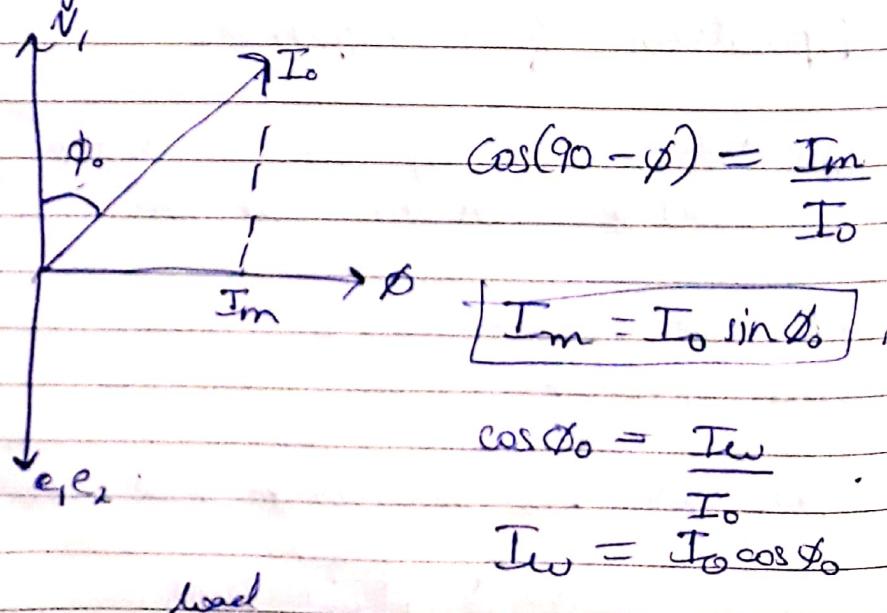

## Load operation of Transformer

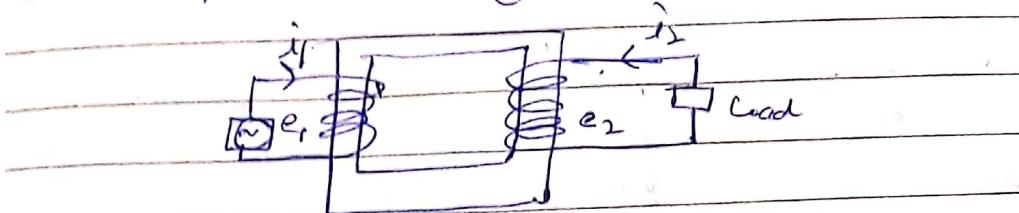

Constant flux m/c.

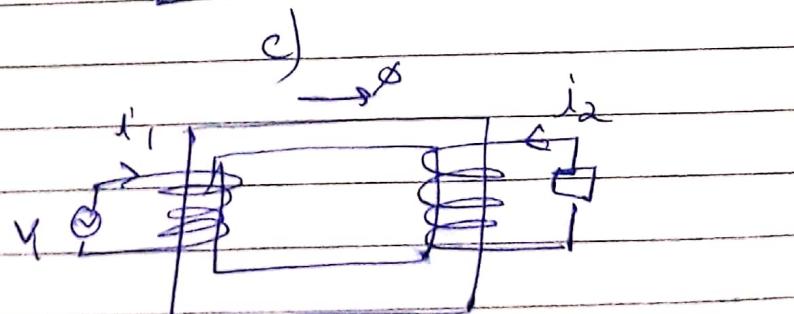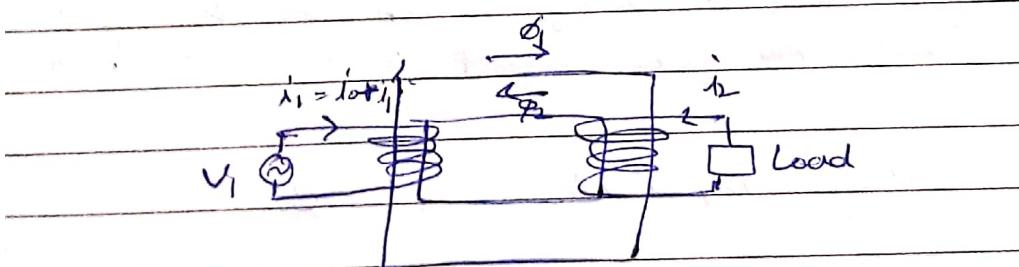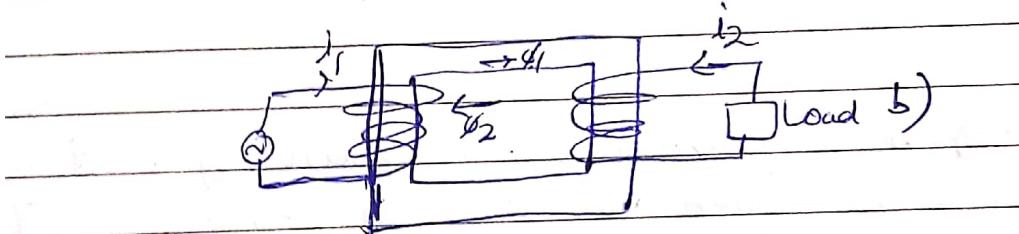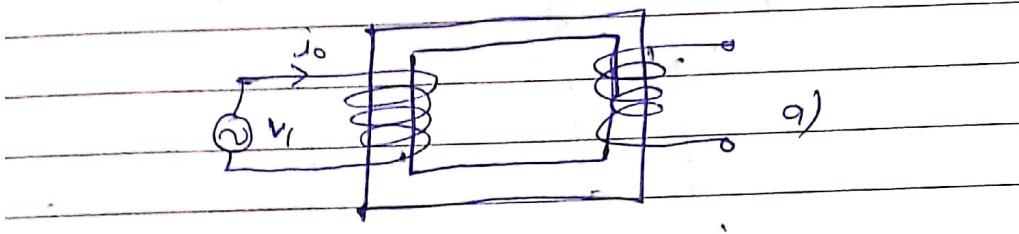


$$V_1 > e_1$$

$$V_1 = e_1 + i_1 R_1 + j i_1 X_1$$

$$e_2 = V_2 + i_2 R_2 + j i_2 X_2$$

→ equivalent CRT:

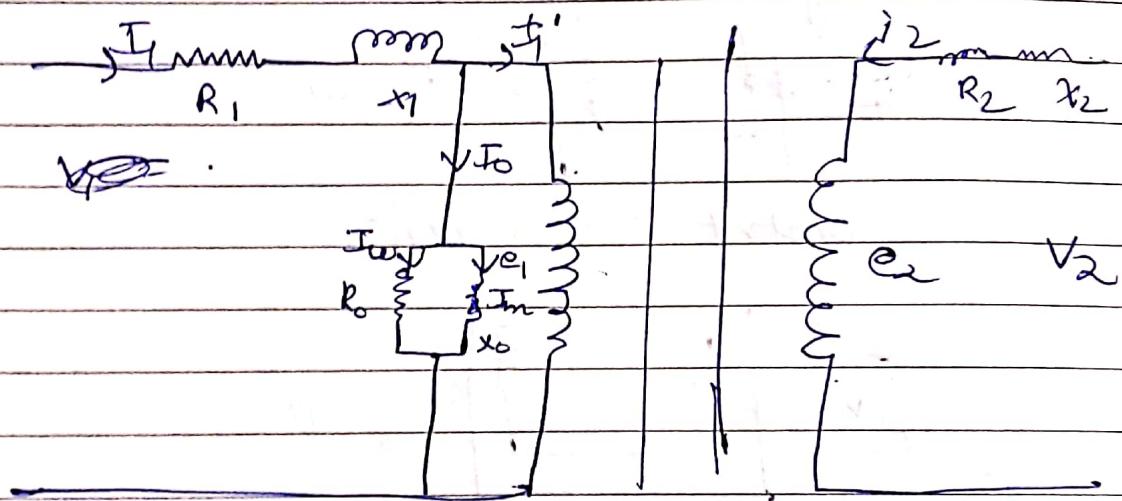

- Q. A transformer primary is drawing  $5A$  under the condition when the sec. is open circuit. Deter the mag. and working component of no load current. Assume at no load current condition the factor is  $0.75$

$$\text{Mag. component} = T_{\text{sinus}}$$